

# HW4

---

## Question 1

---

### Combinational logic

```
@always_comb
def comb():
    # use and or not
    # or use & | ~, but only keep the LSB in the end
    # change the following line to give f correct value
    f.next = (not a and not b and not c and not d) or \
              (a and b and not c and not d) or \
              (not a and b and c and not d) or \
              (not a and not b and c and d) or \
              (a and not b and not c and d) or \
              (a and b and c and d)

    # return the logic
    return comb
```

### Test Cases

```
"/home/mastermind63/Documents/UCONN/Spring 2022/CSE3666/Home  
2022/CSE3666/Homework/HW4/hw4-code/q1.py"
```

a	b	c	d		f
0	0	0	0		1
0	0	0	1		0
0	0	1	0		0
0	0	1	1		1
0	1	0	0		0
0	1	0	1		0
0	1	1	0		1
0	1	1	1		0
1	0	0	0		0
1	0	0	1		1
1	0	1	0		0
1	0	1	1		0
1	1	0	0		1
1	1	0	1		0
1	1	1	0		0
1	1	1	1		1

## Question 2

---

### State Machine

```
# instantiate a register here.  
reg = Register(state, next_state, clock, reset)  
# next_state is the input and stat is the output  
  
# generate next_state, based on state and b  
~~~~~  
@always_comb  
~~~~~  
def next_state_logic():  
    # TODO
```

```
# We can use if-elif-else statements in Python
if state == 0:
    if b == 1:
        next_state.next = 1
    else:
        next_state.next = 0
elif state == 1:
    if b == 1:
        next_state.next = 0
    else:
        next_state.next = 1

# generate output
@always_comb
def z_logic():
    # TODO
    # generate z from state
    if state == 0:
        z.next = 1
    else:
        z.next = 0
```

## Test Cases

```

→ ~/Documents/UConn/Spring 2022/CSE3666/Homework/HW4/hw4-code python3 q2.py 11010011
b | z v
1 | 0 1
1 | 1 3
0 | 1 6
1 | 0 13
0 | 0 26
0 | 0 52
1 | 1 105
1 | 0 211

```

## Question 5

### Code

```

#s[1] = 0;
#return &s[1];
#}
// return the address of s[1]
uint2decstr:
    # Allocate Space
    addi sp, sp, -8 # make space for data on the stack
    sw a1, 0(sp)    # Save the string on the stack
    sw ra, 4(sp)    # Save the return address on the stack

    # Choose to jump to calculate or not
    addi t0, x0, 10 # store the temp value of 10
    bltu a1, t0, calculate # if basecase is reached, then jump to calculate

    # Finish recursion
    divu a1, a1, t0 # divide by 10 and store the result in a1
    jal ra, uint2decstr # Recurse

calculate:
    # Load the values
    lw ra, 4(sp)    # Restore the return address
    lw a1, 0(sp)    # load a0 with the string stored on the stack

    # Test and convert
    addi t0, x0, 10 # store the value of 10 to test against
    remu t1, a1, t0 # take the remainder of v/10
    addi t0, t1, '0' # convert the remainder to a character

    # Store the character conversion
    sb t0, 0(a0)    # store the char in the stack
    addi a0, a0, 1  # increment the address by 1
    addi sp, sp, 8  # restore the stack pointer to where it was

    # Jump
    jr      ra

```

