

Digital Logic Design : Sequential Circuit



Caiwen Ding

Department of Computer Science and Engineering
University of Connecticut

Based on materials from Computer Organization: the Hardware/Software Interface by
D. Patterson and J. Hennessy

Appendix A

- Clock
- Memory elements
 - D Flip-flops, registers, register file
- State machines and timing

G	M	K	unit	m	u	n
10^9	10^6	10^3	10^0	10^{-3}	10^{-6}	10^{-9}

Reading: Sections A.7 - A.11

Combinational versus sequential

Two types of circuit:


- **Combinational circuit**: the outputs depend on the **current** input values
- **Sequential circuit**: the outputs also depend on the **history** of inputs
 - Two identical sequential circuits may produce different outputs even if their current inputs are the same

Clock

- A clock signal oscillates between high and low values
- The clock period is the time for one full cycle
 - Also called **clock cycle time**
 - The **clock rate** is the reciprocal of the cycle time

If the clock cycle time is 1ns, the clock rate is 1 GHz.

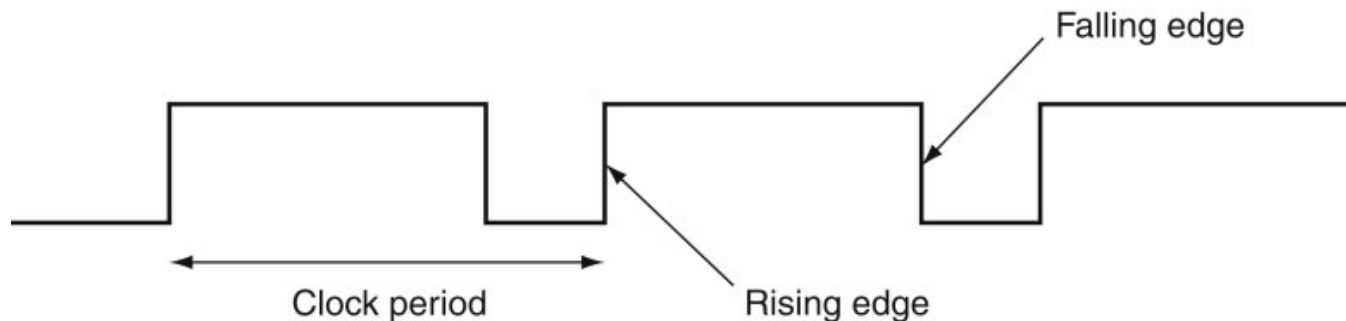If the clock rate is 2 GHz, the clock cycle time is 0.5ns.



Question

If a processor runs at 200 MHz, what is the clock cycle time in ns?

Round to the nearest integer.



- a. 5 ns
- b. 50 ns
- c. 0.5 ns
- d. 500 ns

Why cannot the processor run at higher clock rates?

We are going to see why.

Bistable element

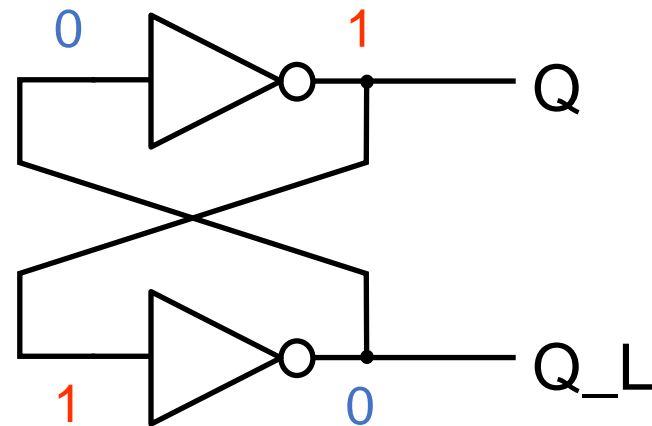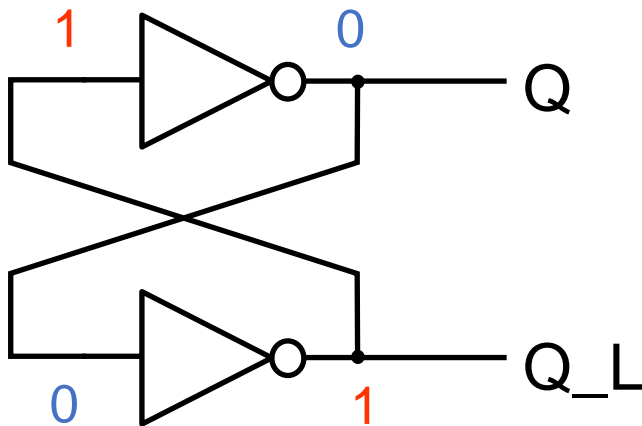- The simplest sequential circuit to remember something
 - Need memory to remember **history** in sequential circuit
- Two states of one state variable
 - For example, Q is 0 or 1



Flip-Flops and Latches

Simplest clocked memory element

Change of state is happened by the clock



Two inputs

Data value (D), clock signal (C)

Two outputs


Value of the state (Q) and its complement ($\sim Q$)

D	C	Q	$\sim Q$
0	0	0	1
1	0	0	1
1	1	1	0
1	0	1	0
0	0	1	0
0	1	0	1
0	0	0	1

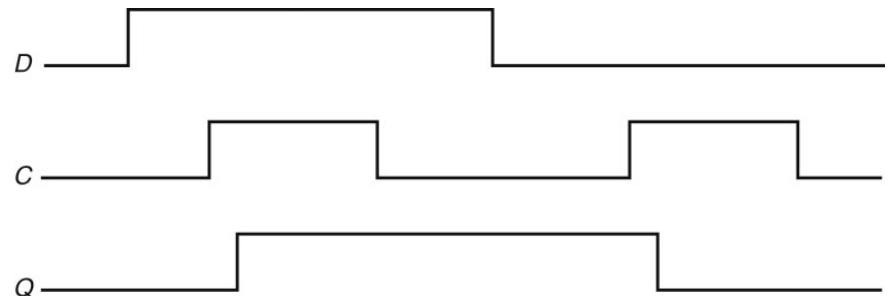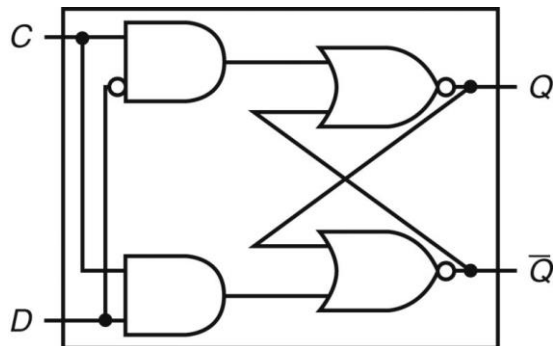

D flip-flop, **positive** edge triggered

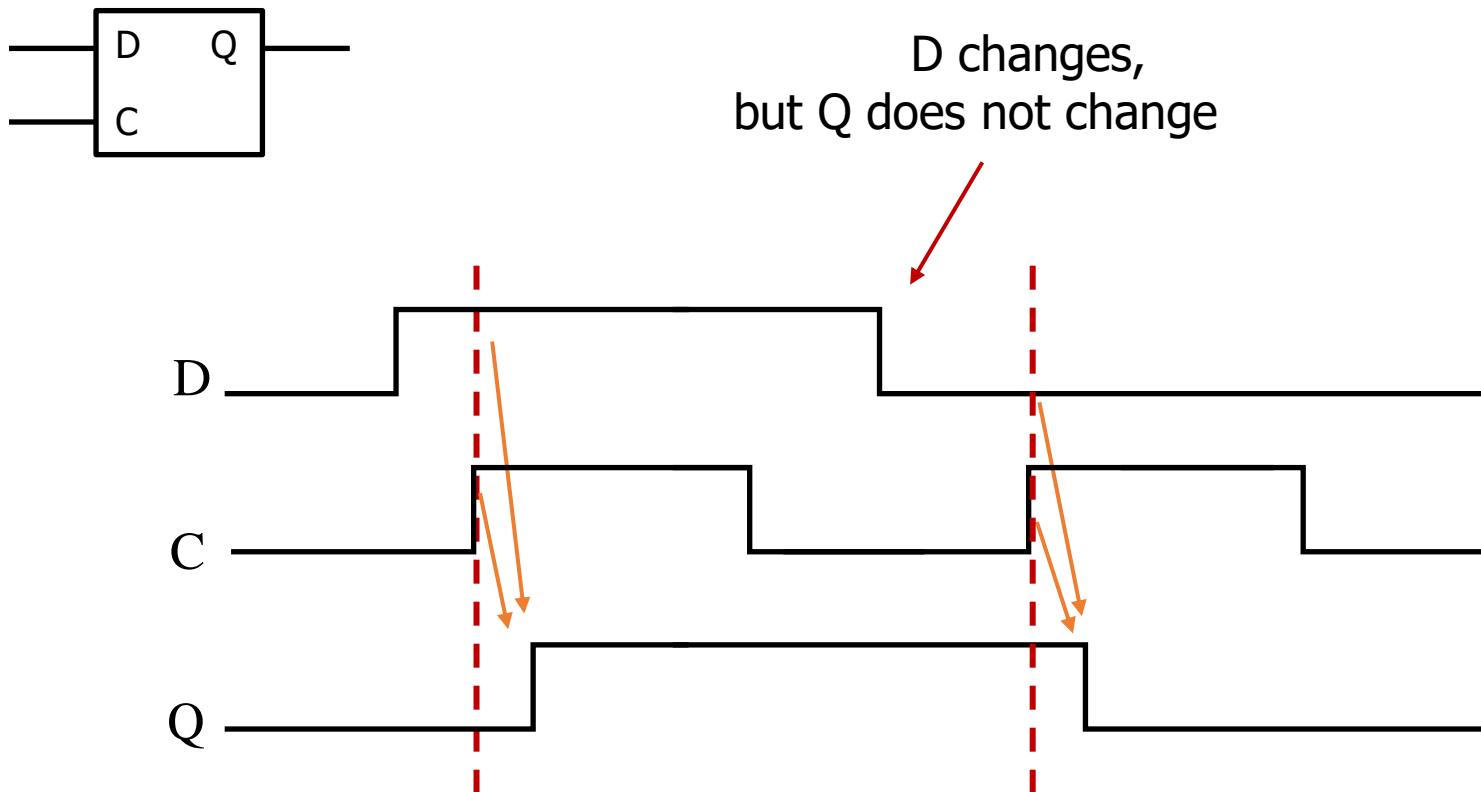- The value of D at the **rising edge** of the control is stored
 - To store a bit in D flip-flop, set up D, and make C transit from 0 to 1




Timing requirements of D Flip-Flop

Setup time: D has to be ready before the edge



Hold time: D has to hold steady for some time after the edge

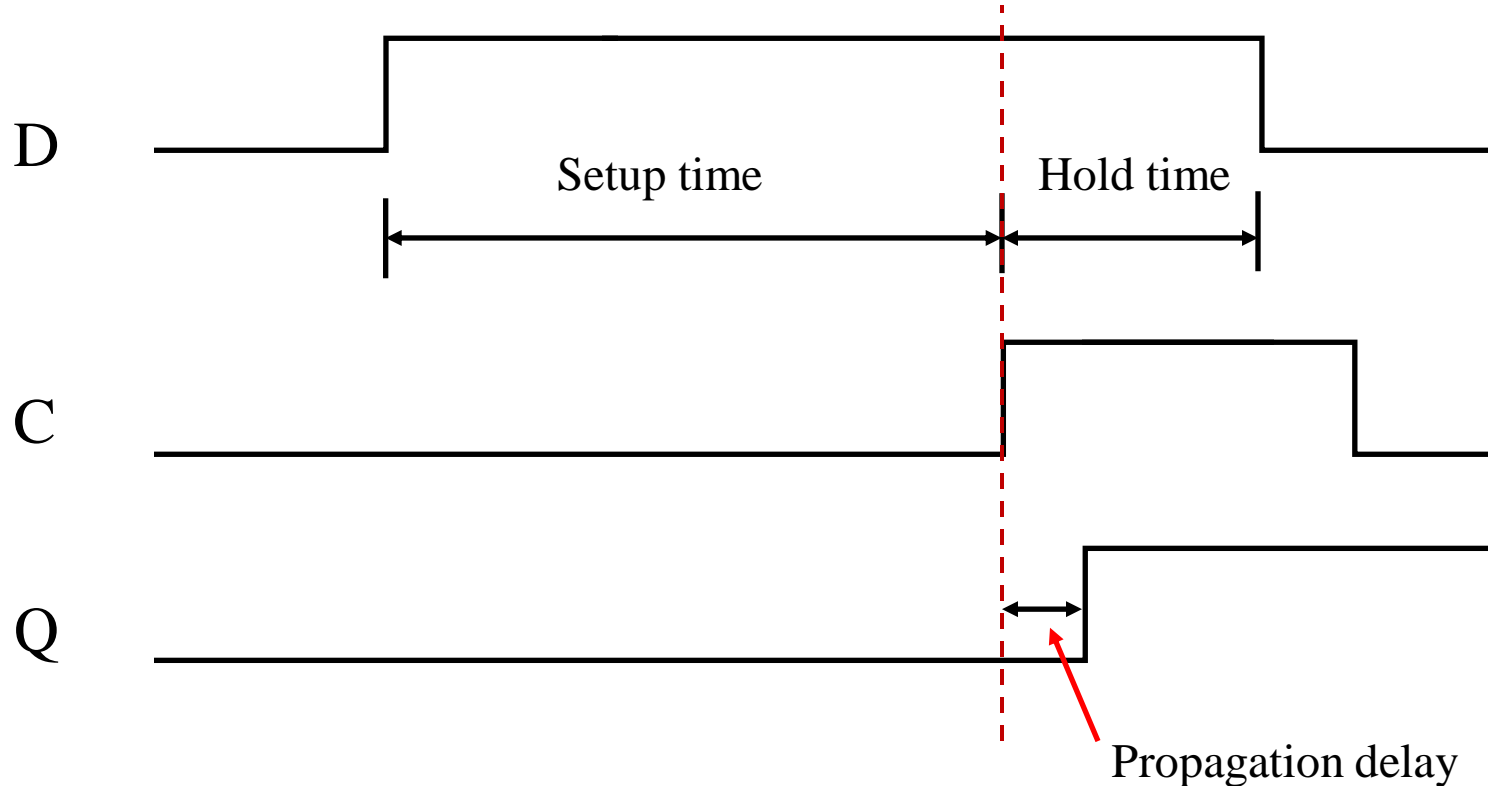Propagation delay: Time for input to propagate to output



Register

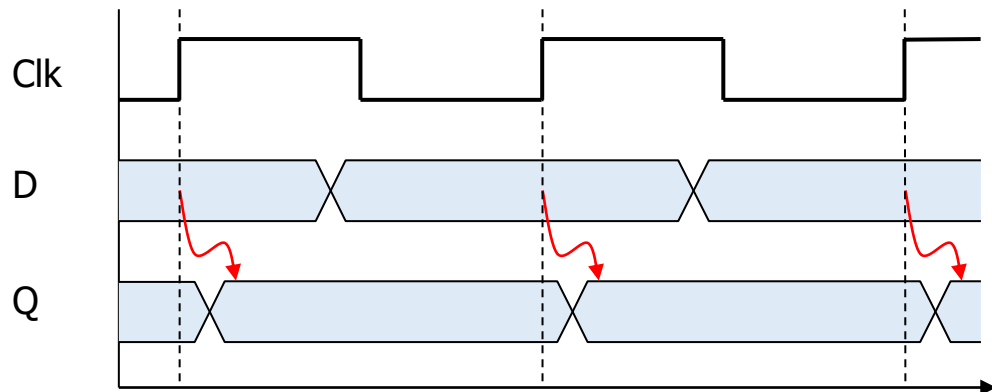
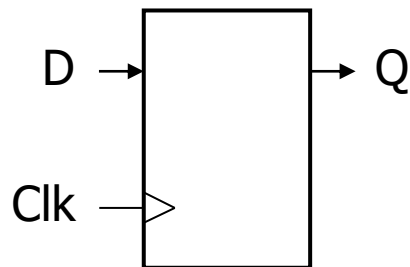
- Register: a memory element that stores data
 - Can be a D flip-flop, or other kind of flip-flops
- A clock signal determines when to update the data
 - The timing diagram below is for a positive edge-triggered register
 - Update happens when clock changes from 0 to 1
- Data stored in registers are steady until next trigger



Register with write control


- The register is updated with D on clock edge **only when write control input is 1**
 - Otherwise, keep the original value in the register

How would you add the Write control?

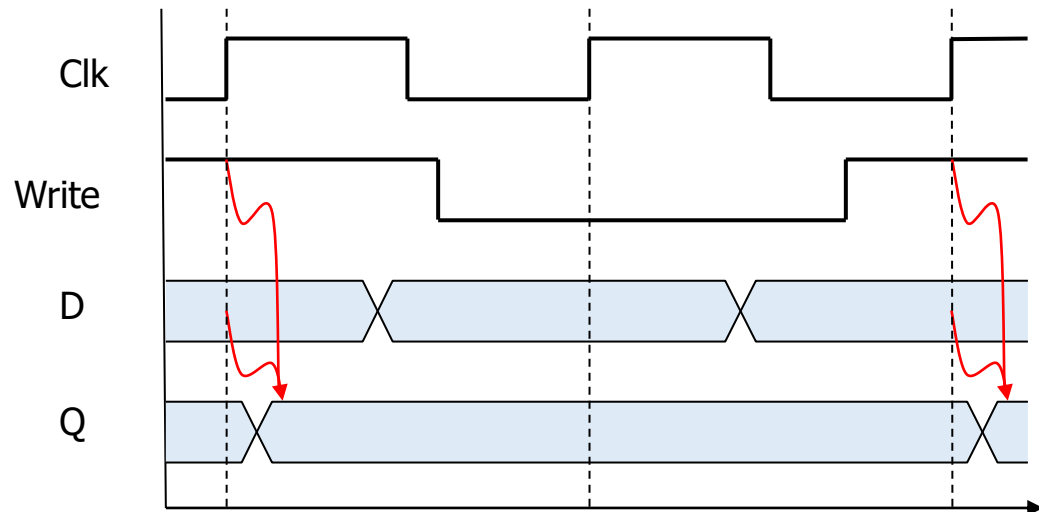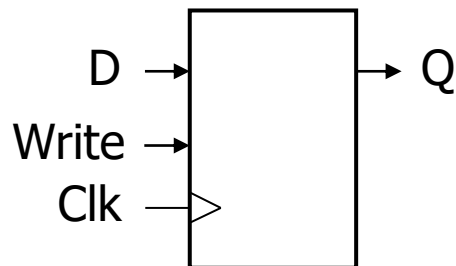

Multibit Register

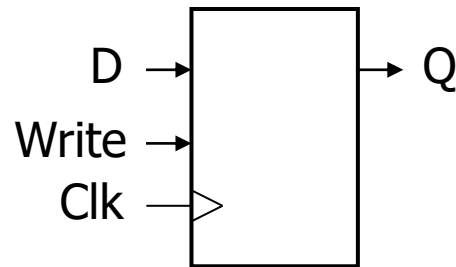- But that's only 1 bit
- How would you build a 32-bit register?




We could use Write to block clock.
It is better to use Write to select one of D and Q

32-bit Register

- An array of 1-bit registers
 - Controlled by the same clock




Remember RISC-V has 32 registers?

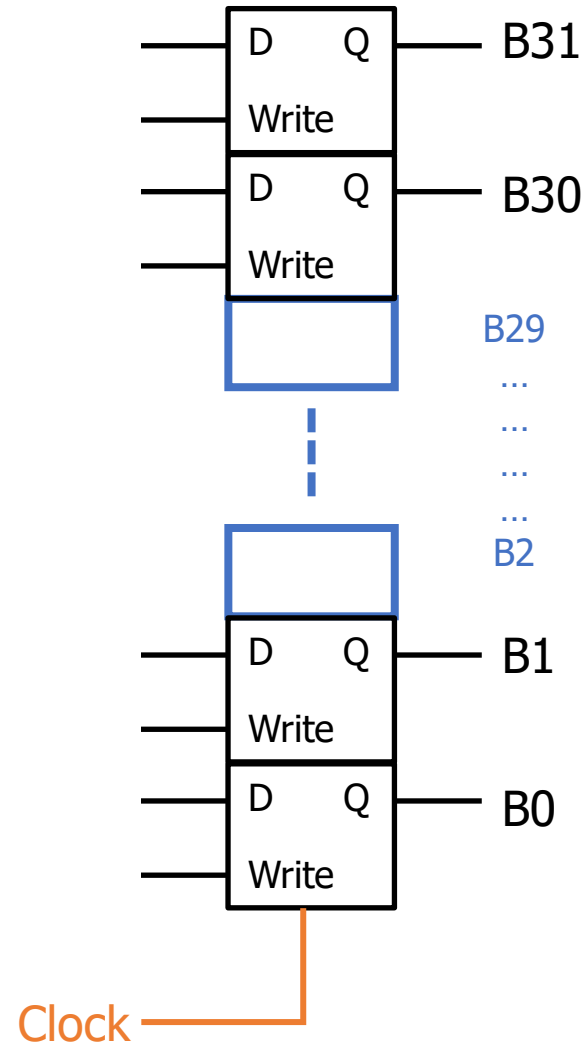


Register File

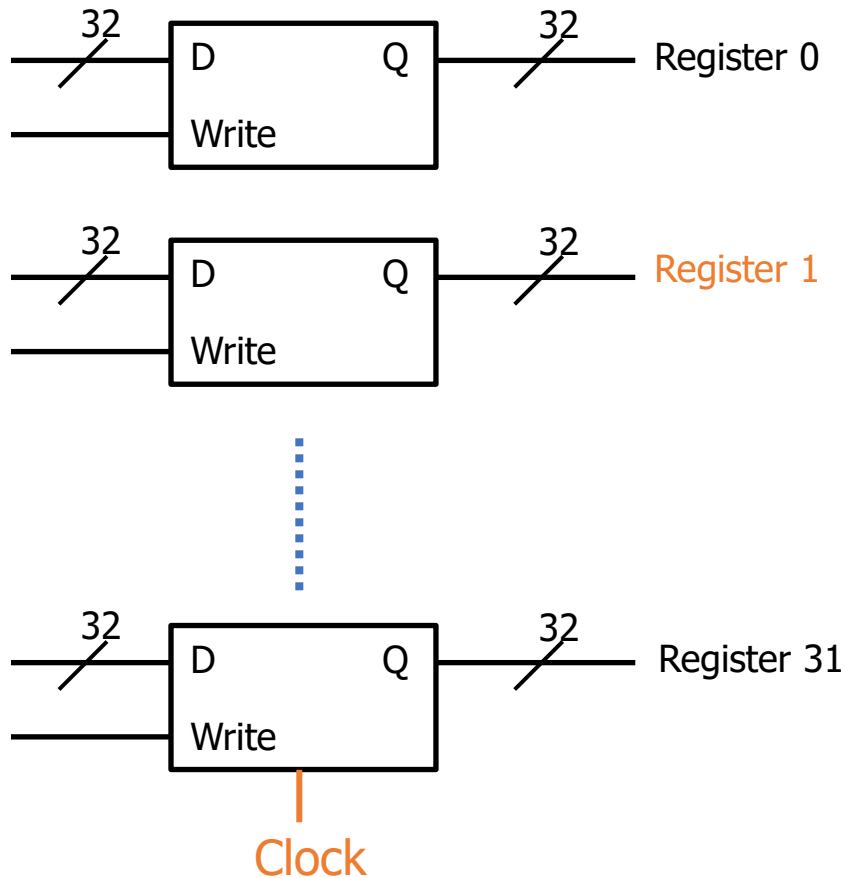- The register file has 32 32-bit Registers
- How do we select the register we need?



Inside the RF: Read ports

- Two MUXes for Two read ports

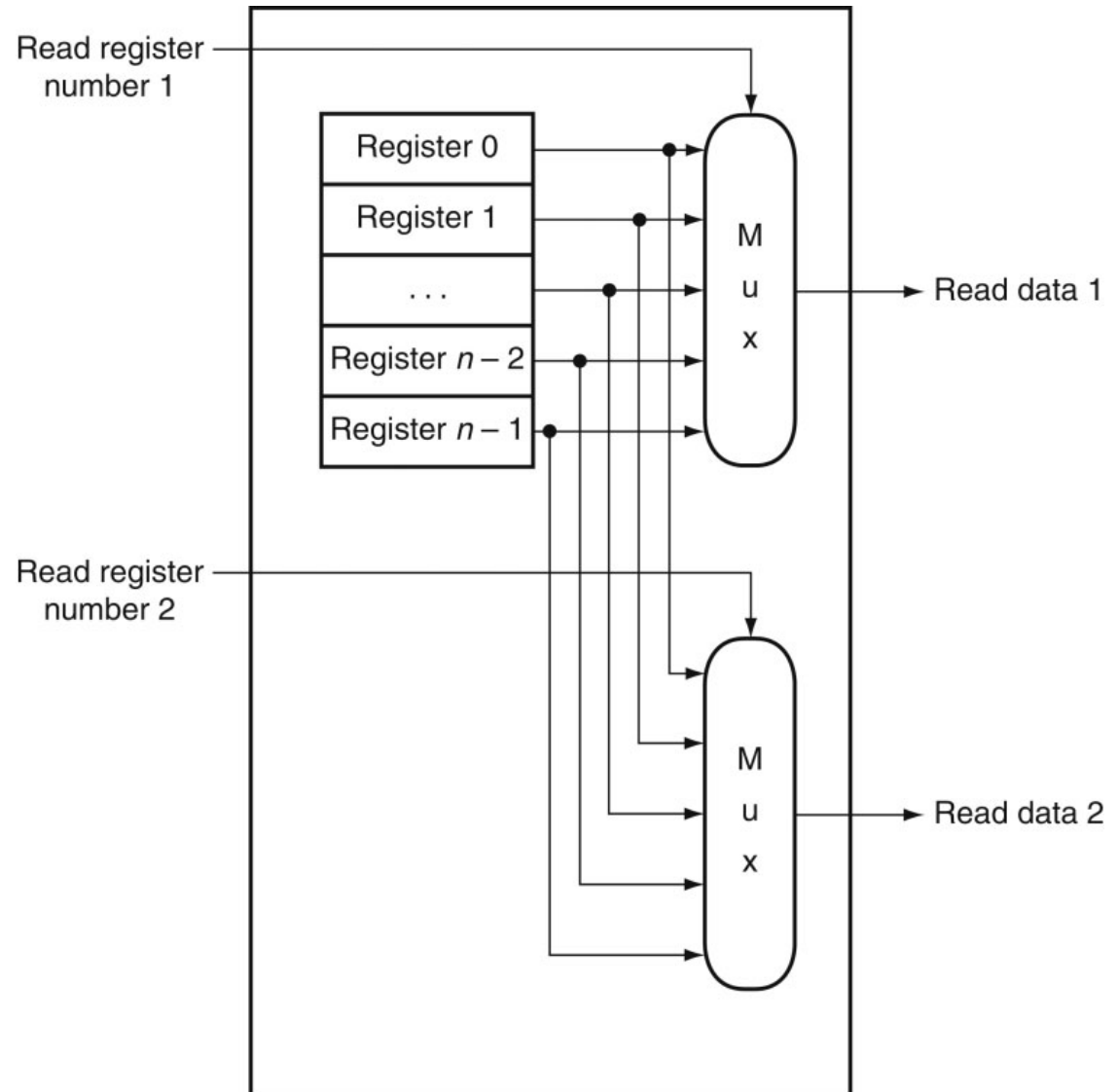


How do we select the register to write?

Inside the RF: Write port

Write goes to AND gates

Register number goes into a decoder, which activates one only register

Register Data are sent to all registers

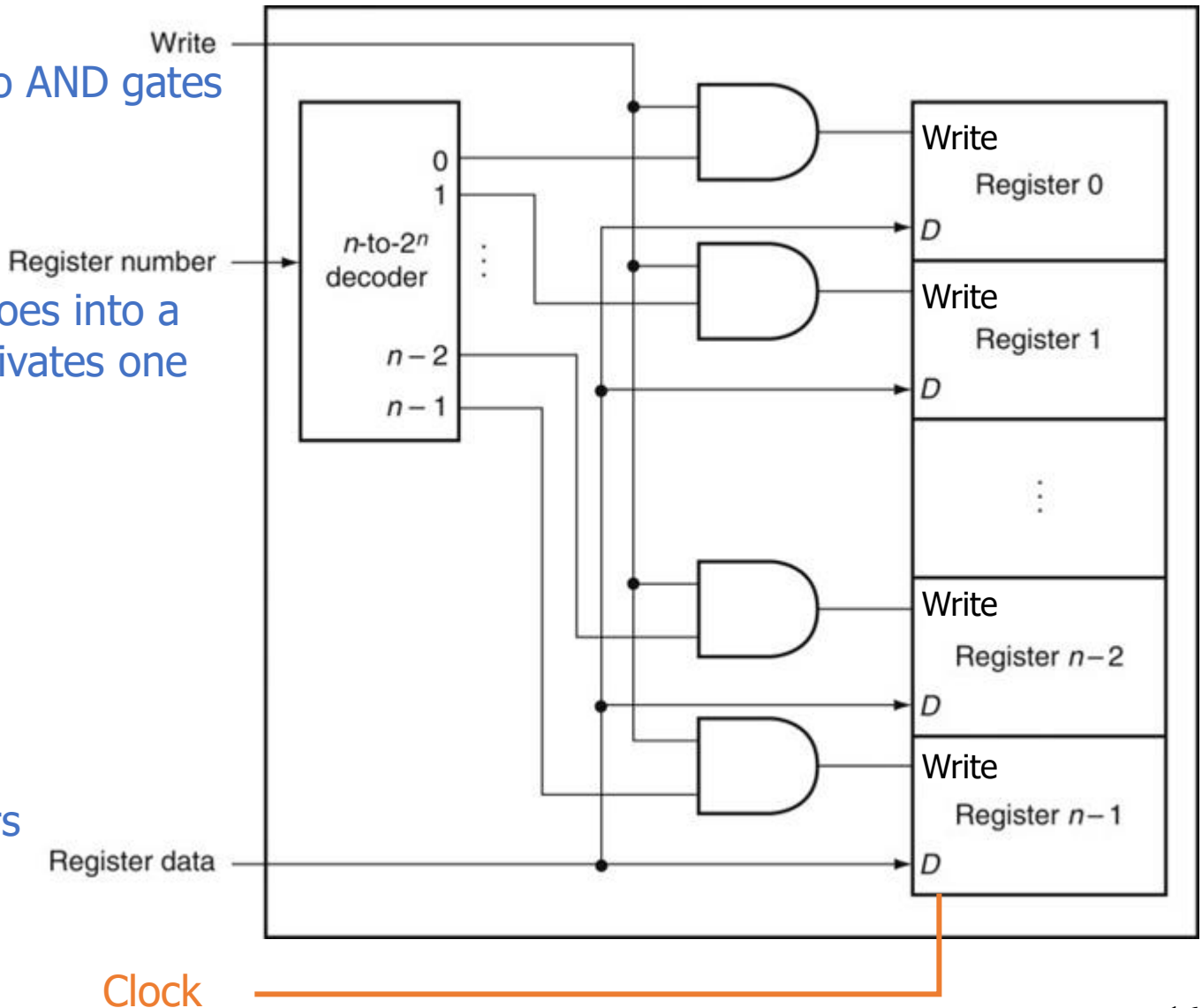

Register File

- Register File (RF) has a collection of registers
- RISC-V RF has 32 32-bit registers
 - Two read ports: can read two registers at the same time
 - One write port
 - Set **Write** to 0 if the instruction does not write to a register


Read

Set read register numbers
Wait for data to be ready

Write

Set write register and write data
Set **Write** to 1
Wait for clock to change


Clock? Not shown.

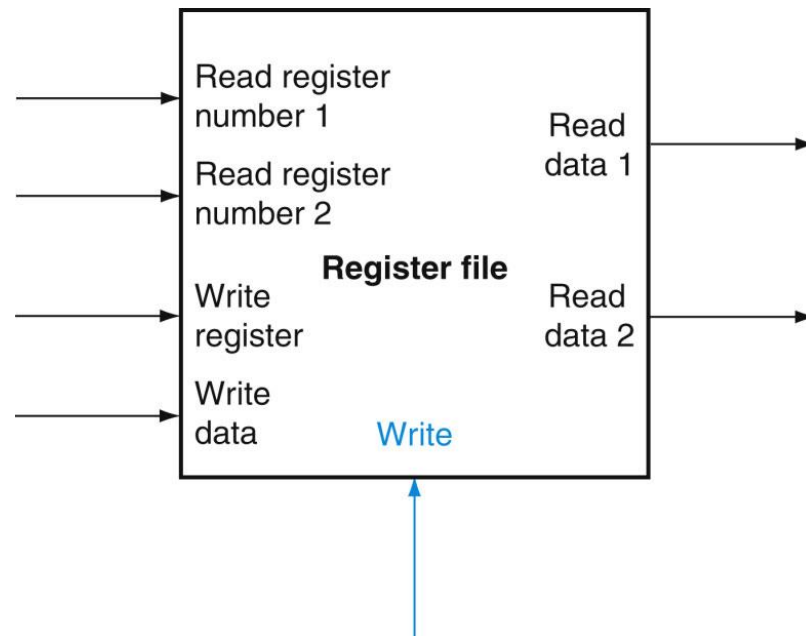

State Machine


- Keeps a summary of previous inputs as state
- In each state, according to the current input,
 - Generate output, which depends on the current state and current input
 - Transit to a new state

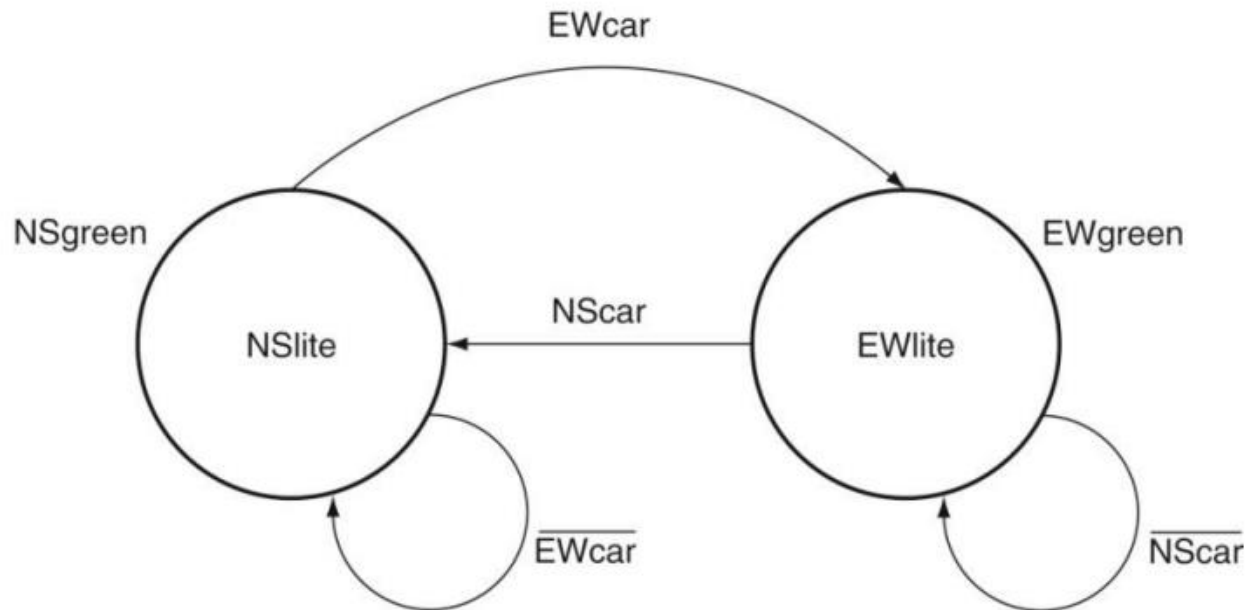State diagram/table describes the behavior of a state machine




Components in a State Machine

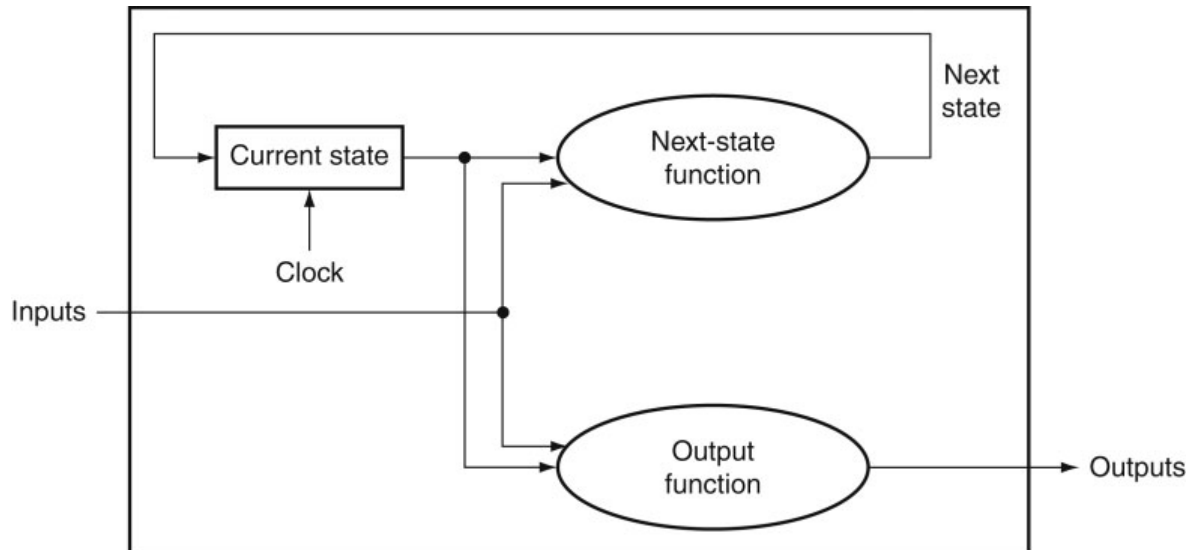- A state machine consists of
 - Memory elements that keep the state
 - Commonly use edge-triggered memory elements
 - All bits are updated at the clock edges and kept steady during the cycle
 - Two combinational functions
 - One generates output
 - One generates the next-state, which will be saved in memory elements when triggered




What is happening in a cycle

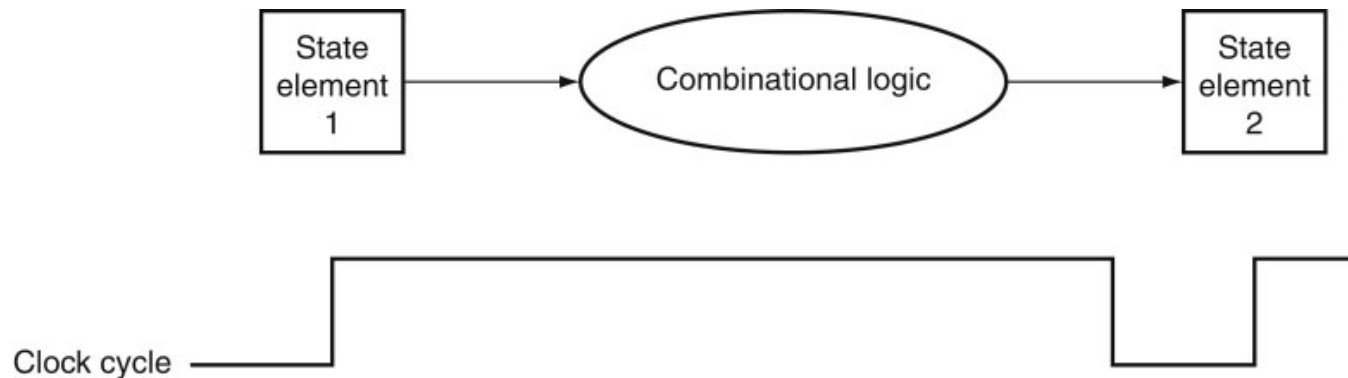- Between clock edges:
 - New state is stored in the state elements
 - Combinational logic computes
 - State for next cycle is presented at the input of the state elements
- The clock cycle must be long enough to complete all work



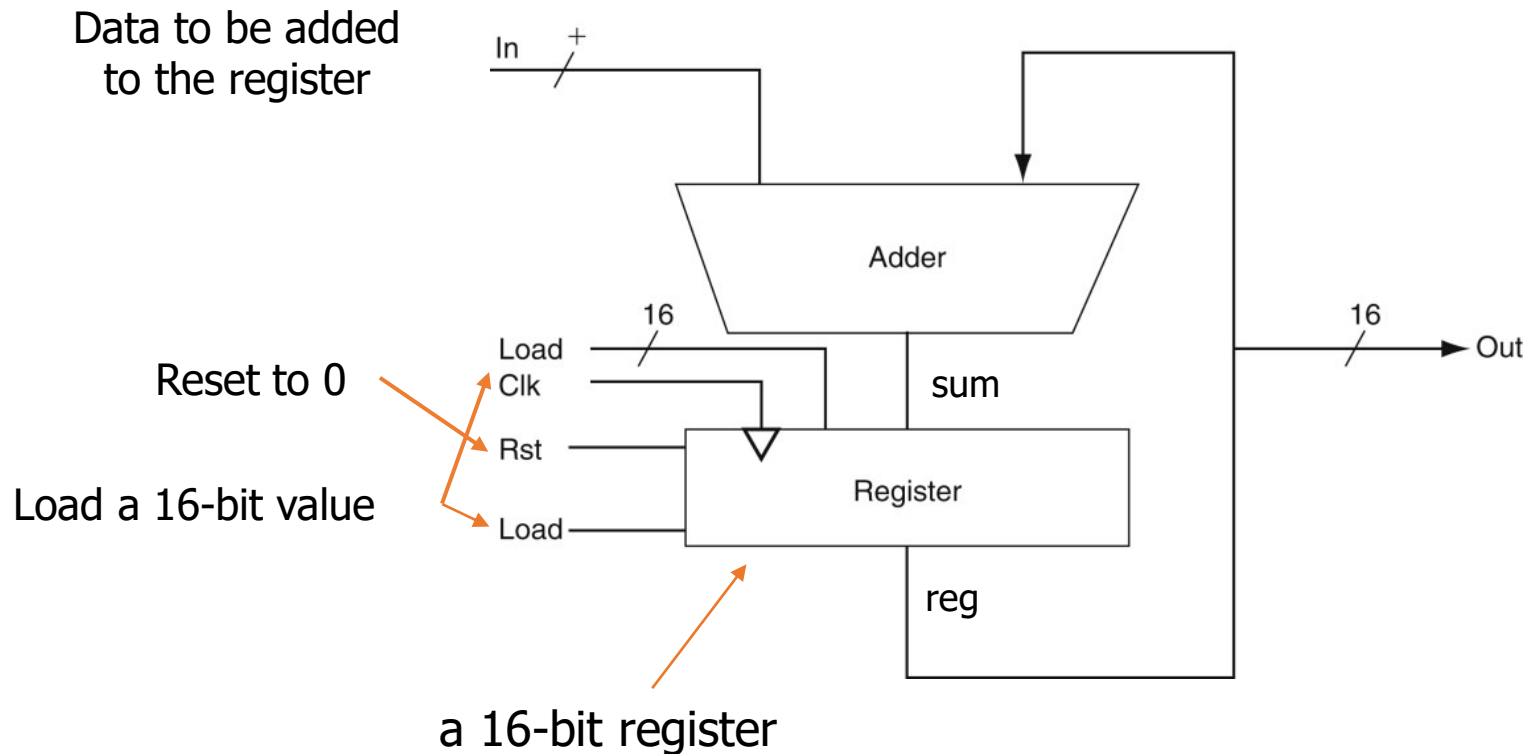
Example: a 16-bit Accumulator

- Add an input number to the existing value in the register
 - If In is 1, the accumulator works as a counter



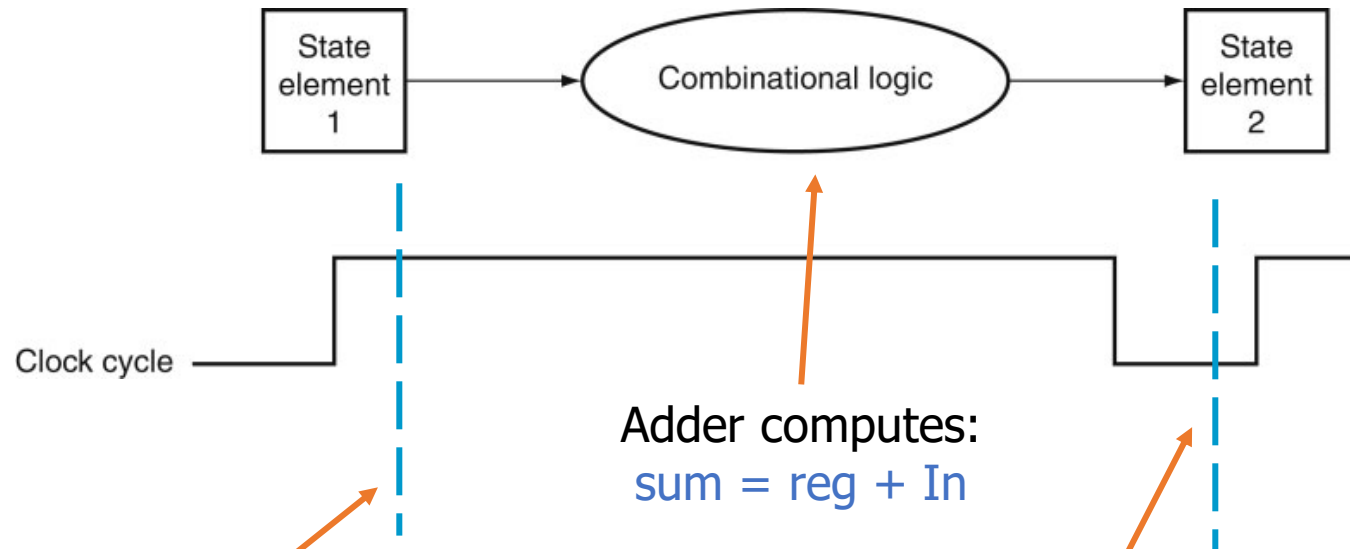Example of a 16-bit Accumulator

- What happens in a cycle (when accumulating)?




After some delay,
the register value is updated

sum presented at the register input
Must be early enough
Otherwise, Res misses the rising edge

Clock Rate

The clock cycle must be longer than the sum of the following delays

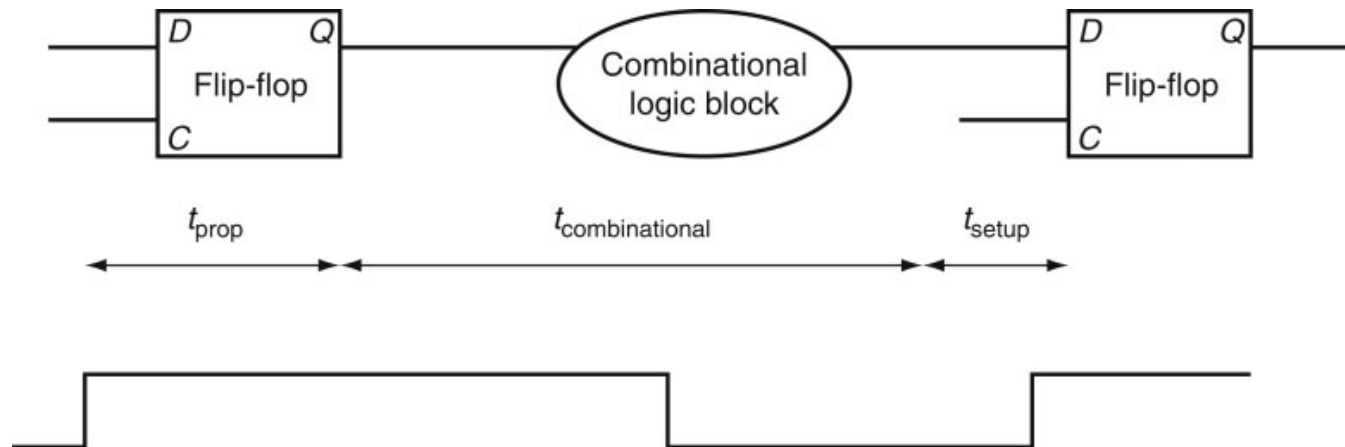- t_{prop} : The time for a flip-flop to propagate input to the output;
- $t_{\text{combinational}}$: The time for the combinational logic to work;
- t_{setup} : New state must arrive early enough to meet the setup requirement




Design of memory

- **Memory** provides a large storage for processors
- Conceptually, memory is just a large register file, but it is very large, which changes many design decisions
 - Each cell (for a bit) must be small and cheap
 - Not using flip-flops
 - Memory is slow (very slow)
 - Pick one word out of 32 vs one out of 1 billion
 - Memory has its own clock
 - Memory consumes a lot of energy

Memory

- Read
 - Set **Address** and **MemRead** (to 1), and wait
 - Get the data from **Read data**
- Write
 - Set **Address**, **Write data**, and **MemWrite** (to 1), and wait

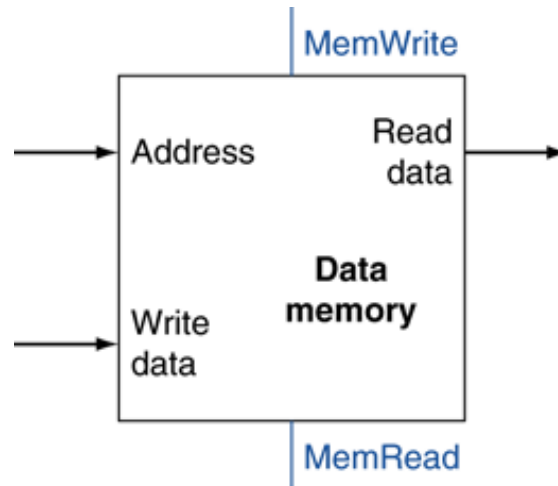
MemWrite and MemRead should not be 1 at the same time



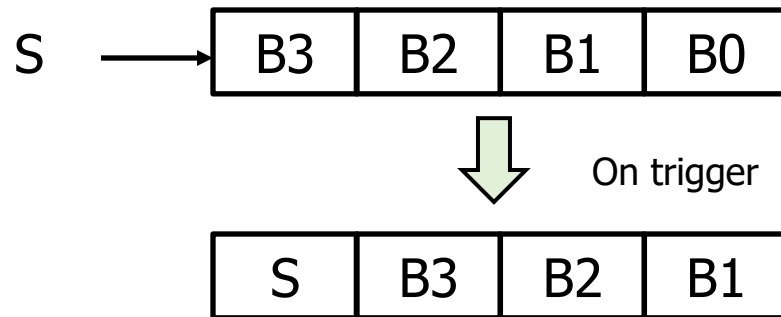Example: Shift Register

- Registers that can shift bits to right (or left)
 - A simple state machine

For example: 4-bit shift register (shift right)




Cycle	In	Register			
0	S0	B3	B2	B1	B0
1	S1	S0	B3	B2	B1
2	S2	S1	S0	B3	B2
...					

Example: 4-bit shift register

Shift right

Bits to be stored in the register in the next cycle: (S, B3, B2, B1)

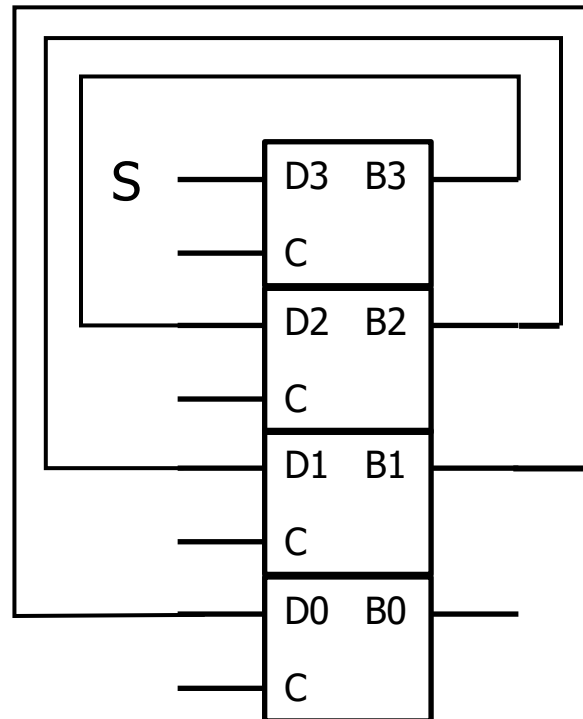- S is connected to D3 because we want S to be stored in bit 3 of the register
- Similarly, B3 is connected to D2, B2 to D1, and B1 to D0



How about shift left?

Clock skew

- Clock arrives at memory elements at different times
 - Also called **timing skew**
- Clock cycle time needs to include the clock skew
 - However, we don't consider it in this course



D flip-flop, **negative** edge triggered

- Negative edge triggered D flip-flop stores D at the **falling edge**

