The Processor: Basic Pipeline



Caiwen Ding
Department of Computer Science and Engineering
University of Connecticut

CSE3666: Introduction to Computer Architecture

Outline

- Concept of pipeline
- Implementation of a 5-stage pipeline

Reading: Sections 4.6 and 4.7.

Skip discussions on hazards in Section 4.6, for now.

Review Clock Cycle Time of Single-Cycle Processor

- Assume time for stages is
 - 100ps for register read or write
 - Main control and register read can be done at the same time
 - 200ps for other stages

7 Clock Cycle						
Instr	Instr V fetch	Register read	ALU op	Memory	Register write	Total time
lw	200ps	100ps	200ps	200ps	100ps	800ps
SW	200ps	100ps	200ps	200ps	(700ps
R-format	/ 200ps	100ps	200ps		100ps	600ps
beq	200ps	100ps	200ps			500ps

Performance Issues with Single-Cycle Implementation

- The cycle time is the same for all instructions
 - Not feasible to vary period for different instructions
- Longest delay determines clock period
 - Critical path: the load (LW) instruction

write to Reg

Instruction memory \rightarrow Register file \rightarrow ALU \rightarrow Data memory \rightarrow Register file/

- Violates design principle
 - Making the common case fast
- How can we improve the performance?

Five steps in RISC-V instruction execution

Observations in the single-cycle RISC-V execution.

The execution of an instruction has five important steps:

- 1. Fetch instruction from memory (IF)
- 2. Read register file and decode instructions (ID)
- 3. Use ALU to compare numbers or to compute results/addresses (EX)
- 4. Access data memory (MEM)
- 5. Write the result into register (WB)


Another Important Observation

- An instruction does not need to do all stages at the same time.
 - A hardware module is idle in most part of a cycle.

Instruction memory \rightarrow Register file \rightarrow ALU \rightarrow Data memory \rightarrow Register file


For example, an instruction only uses I-Mem at beginning of a cycle.

When it uses ALU, I Mem is idle.

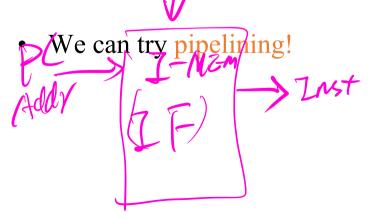


• 4-step laundry:

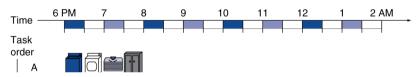- Place one dirty load of clothes in the washer.
- When the washer is finished, place the wet load in the dryer.
- When the dryer is finished, place the dry load on a table and fold.
- When folding is finished, ask your roommate to take out the clothes.




1 task: 4 steps (2 hours)

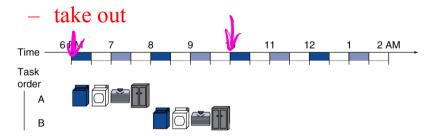
- Laundry: multiple tasks
 - washer
 - dryer
 - fold



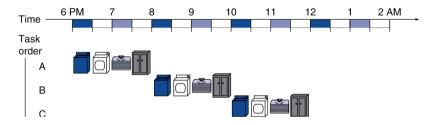- Laundry: Multiple loads
 - washer
 - dryer
 - fold
 - take out



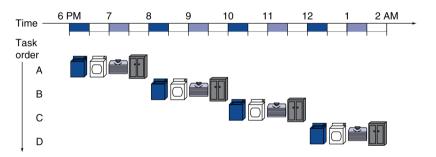- Laundry: Multiple tasks
 - washer
 - dryer
 - fold
 - take out




Execution time of Non-stop *n* tasks: 4*n*

4 tasks (6pm – 2am)

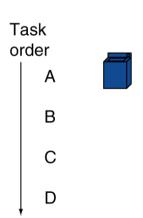
Question: how many "hardware" do we have?








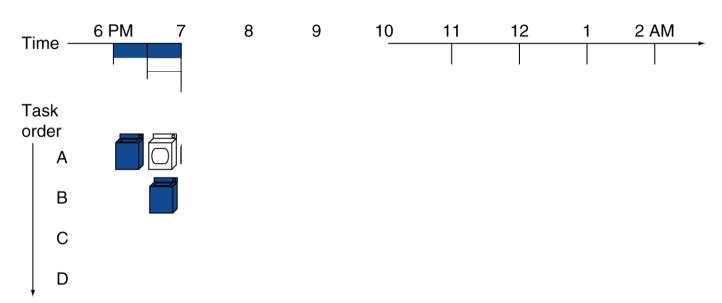
• Pipelined laundry: overlapping execution




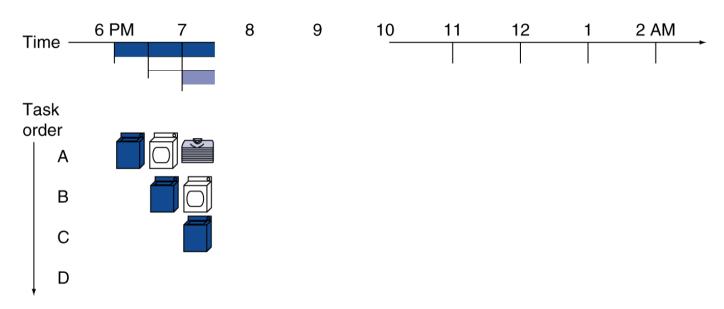
Question: how many "hardware" do we have?







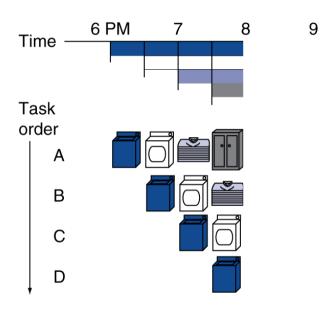


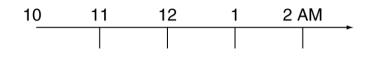


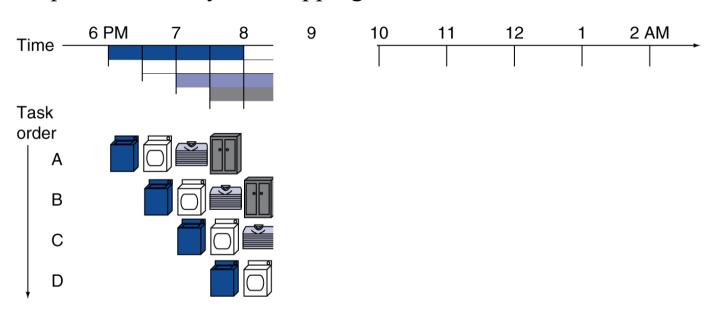

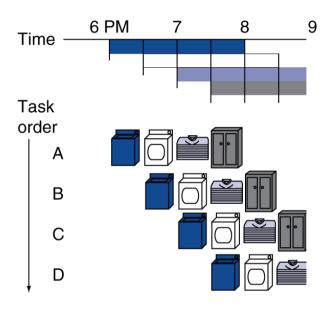


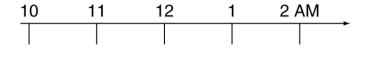


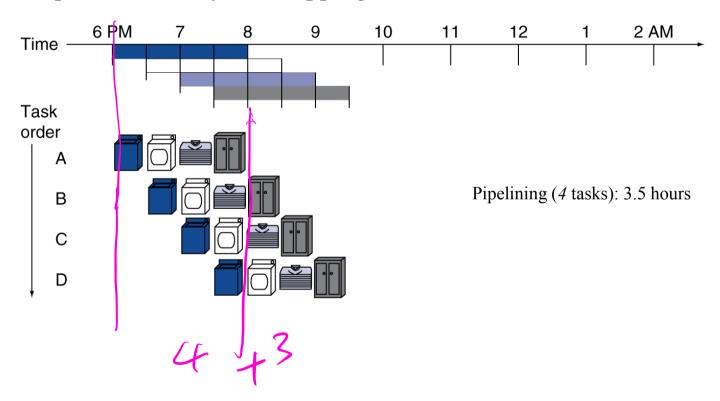

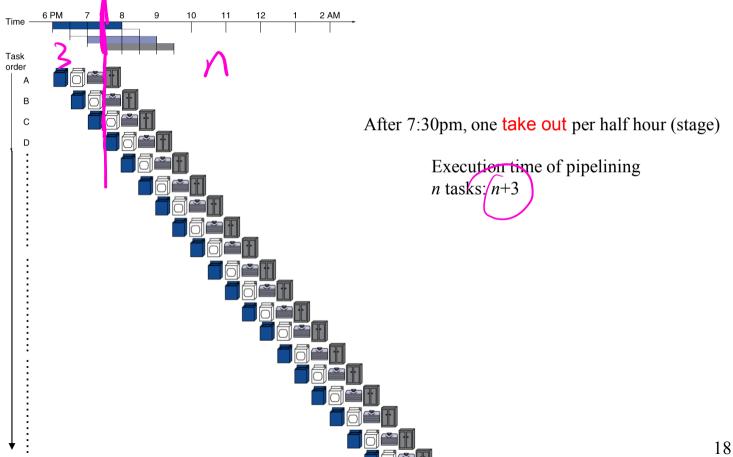

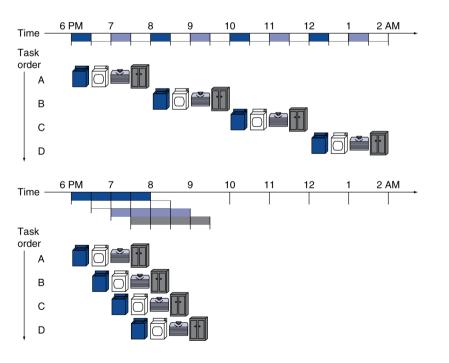- Pipelined laundry: overlapping execution
 - Parallelism improves performance
 - Do you see the parallelism in the figures?




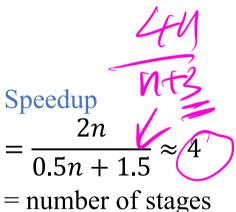





Create a pipeline of five stages, one step per stage.

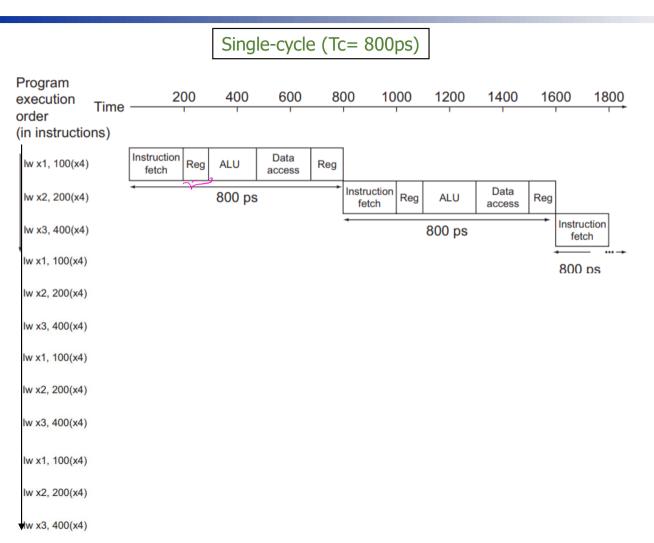
- 1. IF: Instruction fetch from memory
- 2. ID: Instruction decode & register read
- 3. EX: Execute operation or calculate address
- 4. MEM: Access memory operand
- 5. WB: Write result back to register



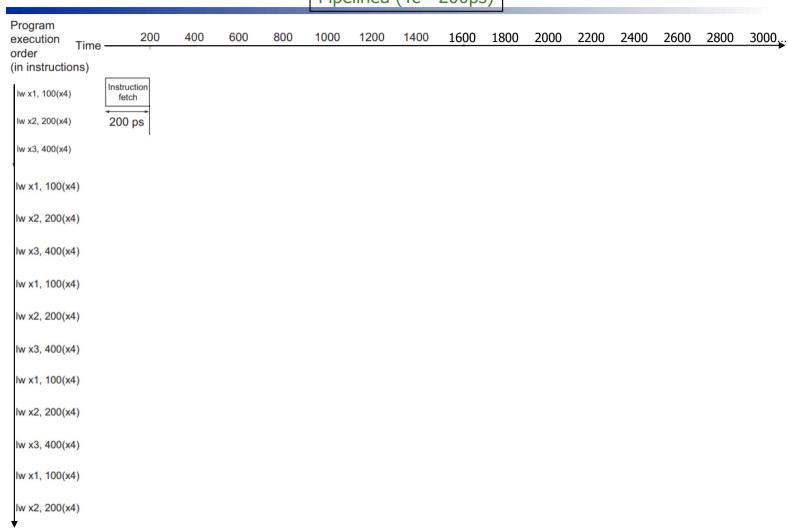

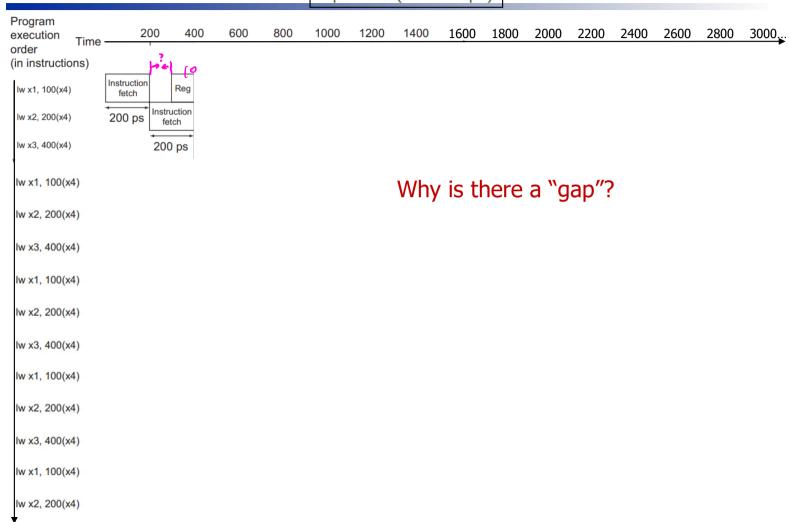

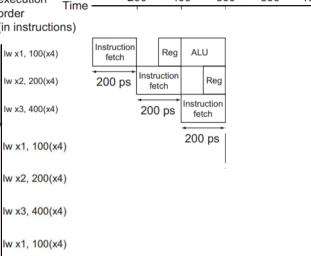Pipeline Performance Pipelined (Tc= 200ps) **Program** 3000... 200 400 600 800 1000 1200 1400 1600 1800 2000 2200 2400 2600 2800 execution Time order (in instructions) Instruction Reg ALU lw x1, 100(x4) fetch



lw x2, 200(x4)

lw x3, 400(x4)

lw x1, 100(x4)


lw x2, 200(x4)


lw x3, 400(x4)


lw x1, 100(x4)


lw x2, 200(x4)


Why is there a "gap"?

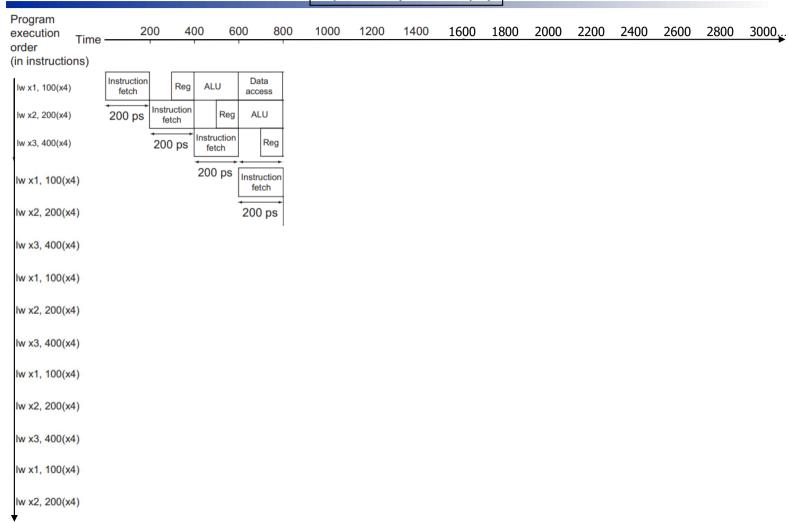


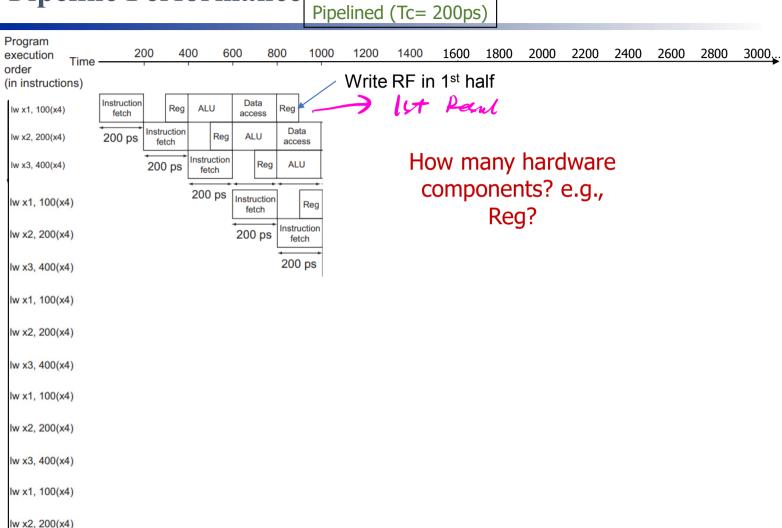


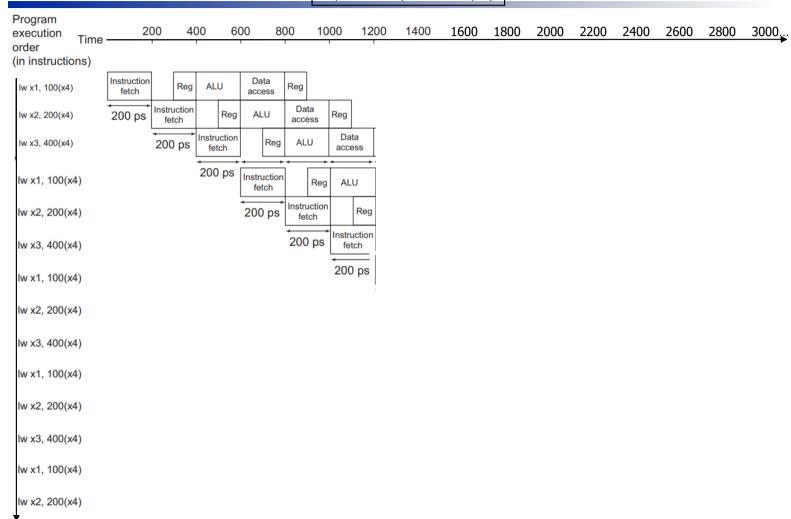


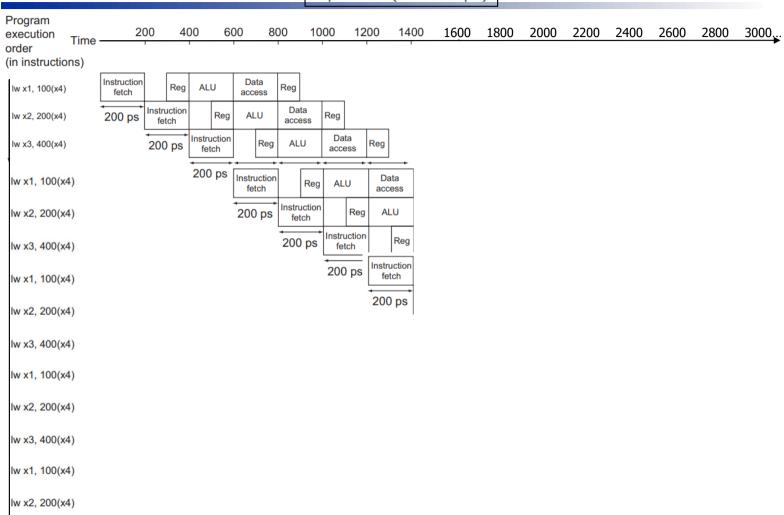


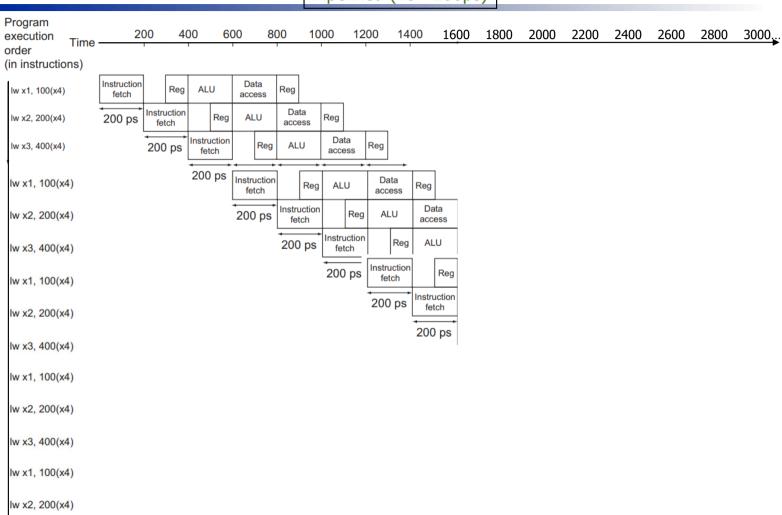


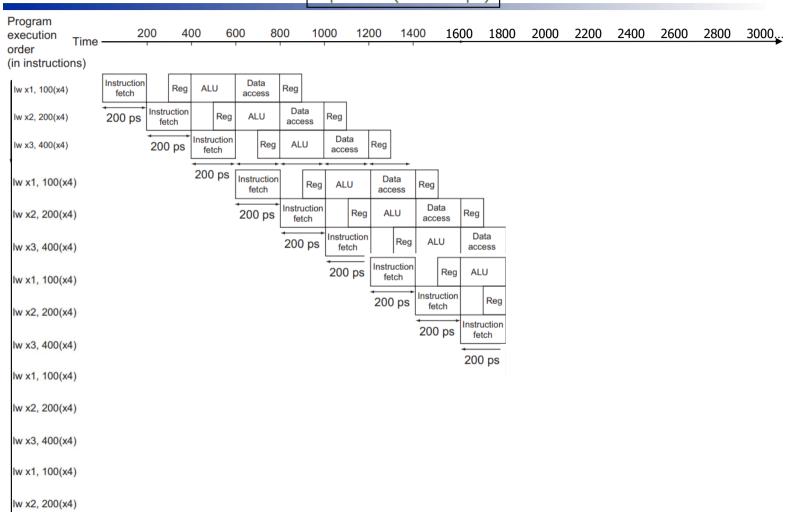


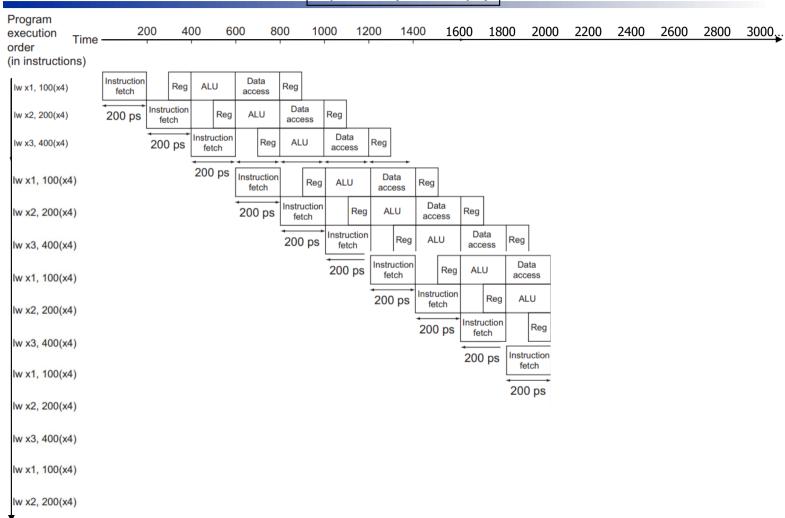


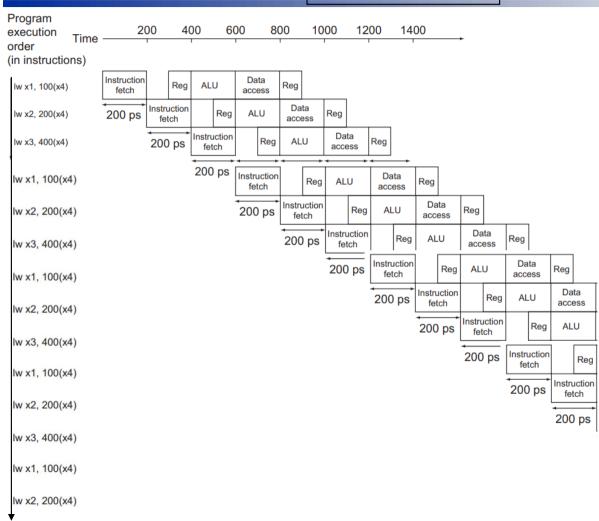

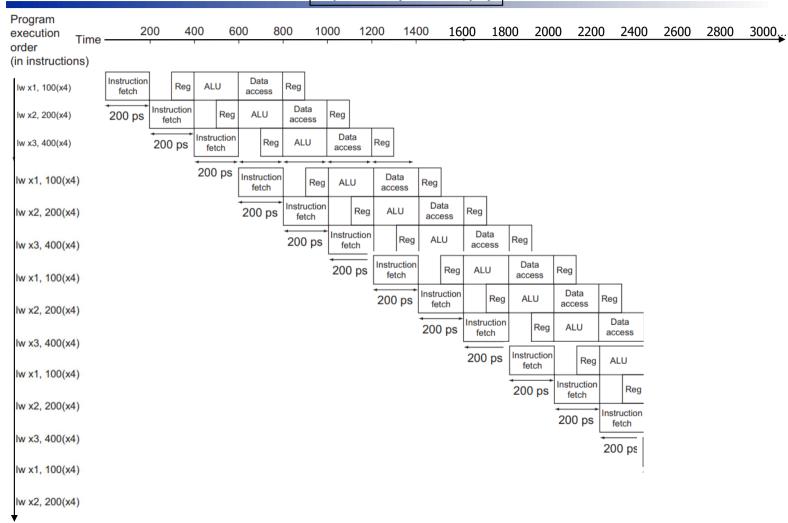

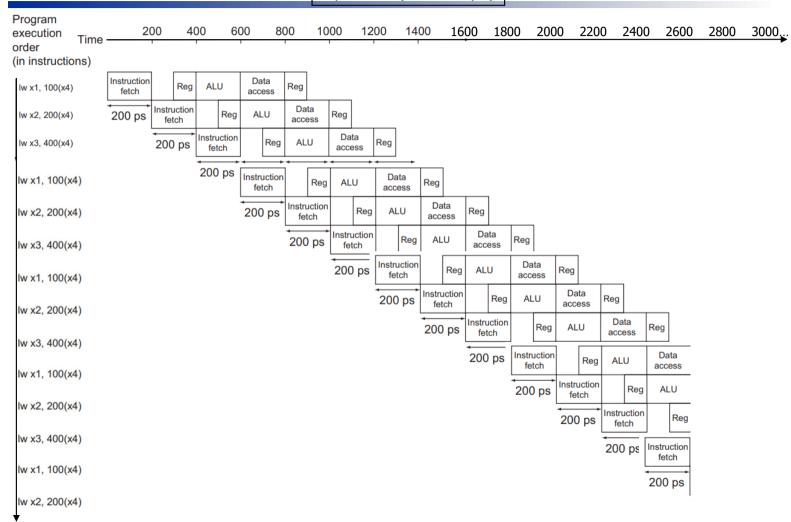

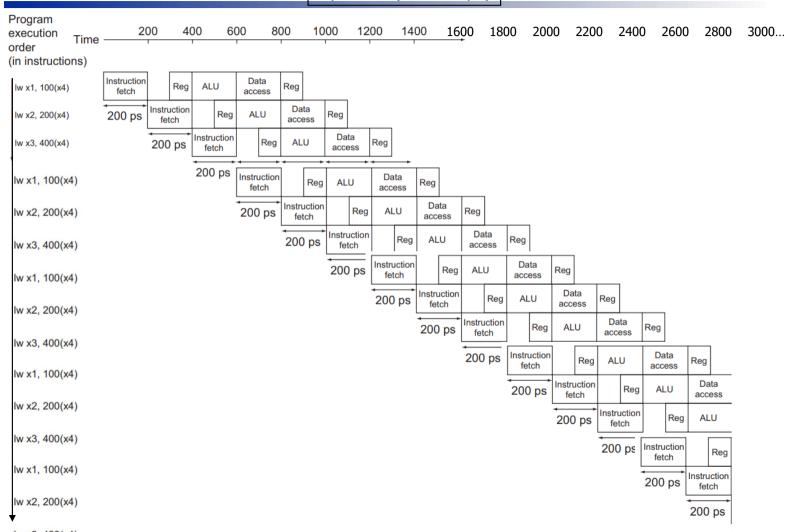

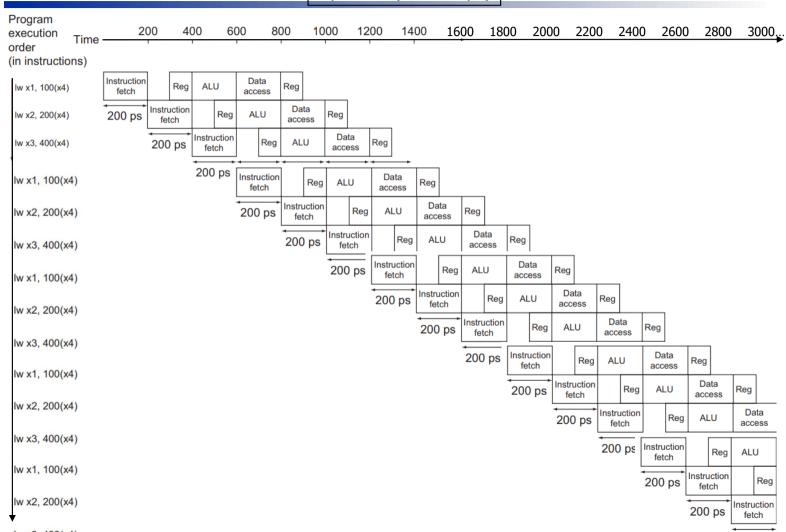

Pipeline Performance Single-cycle (Tc= \$00ps) **Program** 200 800 1000 1200 1400 1600 600 1800 execution Time order (in instructions) Instruction Data lw x1, 100(x4) Reg ALU Reg fetch access Instruction Data 800 ps lw x2, 200(x4) Reg ALU Reg fetch access Instruction 800 ps lw x3, 400(x4) fetch 800 ps Pipelined (Tc= 200ps) **Program** 800 200 400 600 1000 1200 1400 execution Time order (in instructions) Instruction Data ALU Reg lw x1, 100(x4) fetcl access Write RF in 1st half Instruction Data lw x2, 200(x4) 200 ps Reg ALU Reg fetch access Instruction Data lw x3, 400(x4) 200 ps Reg ALU Reg fetch access 200 ps 200 ps 200 ps 200 ps 200 ps

What is the speedup for a long instruction sequence?

Ideal Pipeline Speedup

Ideally,

$$\label{eq:Time Between Instr_nonpipelined} Time \ Between \ Instr_{nonpipelined} = \frac{Time \ Between \ Instr_{nonpipelined}}{Number \ Of \ Stages}$$

$$Speedup = \frac{Time\ Between\ Instr_{nonpipelined}}{Time\ Between\ Instr_{pipelined}} = \ Number\ of\ Stages$$


Actual speedup is less than the ideal speedup, why?

Pipeline Speedup

- Actual speedup is less than the ideal speedup
 - Pipeline stages are not balanced ()
 - Overhead in pipeline
 - Clock skew
 - Hazard
- Speedup due to increased throughput VS (cotency
 - Latency (time for executing each instruction) does not decrease, but increases


I clock cycle -> sing-cycle

RISC-V Datapath Divided in Five Stages

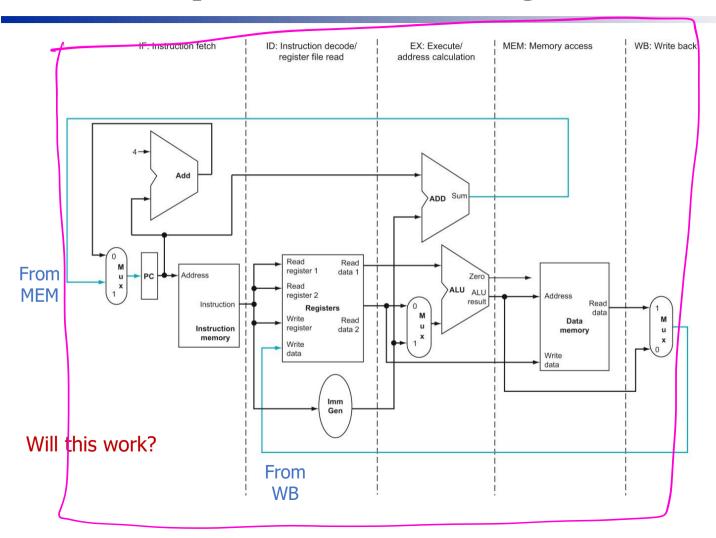

Pipelined Datapath

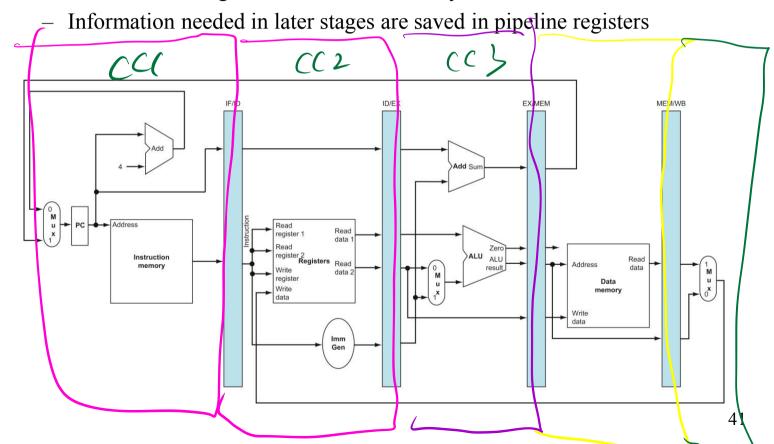- Add pipeline registers between pipeline stages to isolate them
 - Data stored in registers are stable for the cycle



Two rules

no need to memorize!

- In general, we follow the following two rules
 - Do not use the signal generated in the same stage
 - To reduce the cycle time
 - Results are saved in pipeline registers and passed to later stage
 - Use a signal as early as possible
 - We do not need pass it to later stages


Control Signals in Pipeline

- Control signals derived from instruction, as in single-cycle implementation
- All control signals are generated in ID and passed to later stages through the pipeline (also called state) registers
 - 2 used in EX, 3 used in Mem, and 2 in WB


	EX Stage		N	ИЕМ Stage	WB Stage		
	ALUOp	ALUSrc	Branch	Mem Read	Mem Write	Reg Write	Mem toReg
R	10	0	0	0	0	1	0
LW	00	1	0	1	0	1	1
SW	00	1	0	0	1	0	Х
BEQ	01	0	1	0	0	0	Х

Control Signals in Pipeline Registers

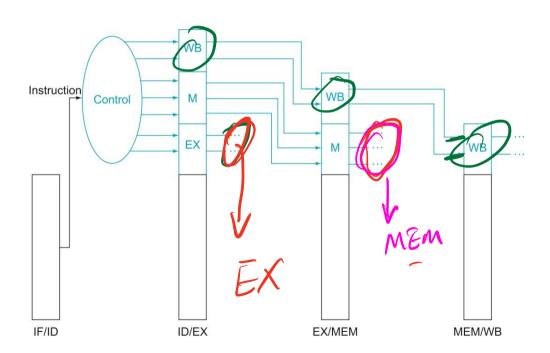• Control signals are generated in ID and passed to later stages



RISC-V Pipeline

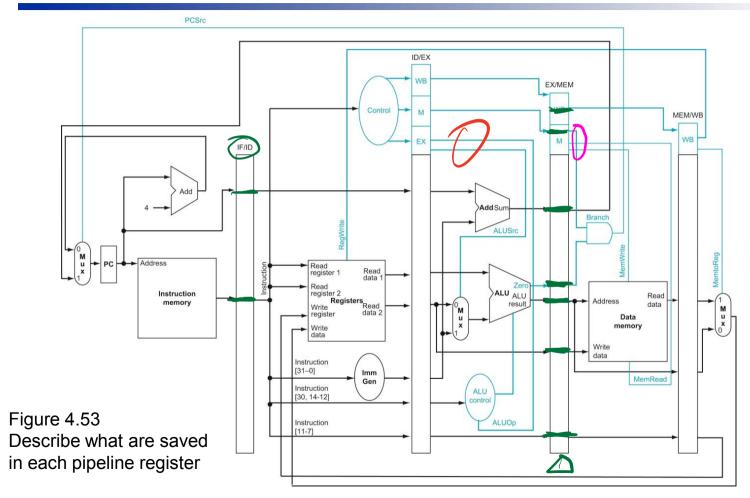

Information saved into pipeline registers

Any info needed in a later stage must be passed to that stage via pipeline registers Study the diagram and check if any signal is missing




- IF/ID
 - PC, Instruction
- ID/EX
 - PC
 - Read data 1, Read data 2, immd, funct3, and rd
 - Control signals
- EX/MEM
 - Read data 2, rd, MemRead, MemWrite, Branch, RegWrite, and MemtoReg
 - ALU result and Zero, Branch target address, Write register
- MEM/WB
 - ALU result, rd, RegWrite, and MemtoReg
 - Mem read data

Pipeline Diagrams


- Can help with answering questions like:
 - How many cycles does it take to execute this code $\frac{150-0}{150}$
 - What is the ALU doing during cycle 4?
 - Is there a hazard, why does it occur, and how can it be fixed?
- Two types of diagrams
 - "Single-clock-cycle" pipeline diagram
 - Shows pipeline usage in a single cycle
 - Highlight resources used
 - "Multi-clock-cycle" pipeline diagram
 - Showing how instructions are executed over time


What we mainly use

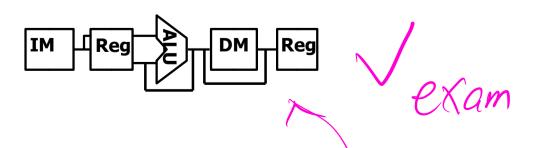



Single-Cycle Pipeline Diagram

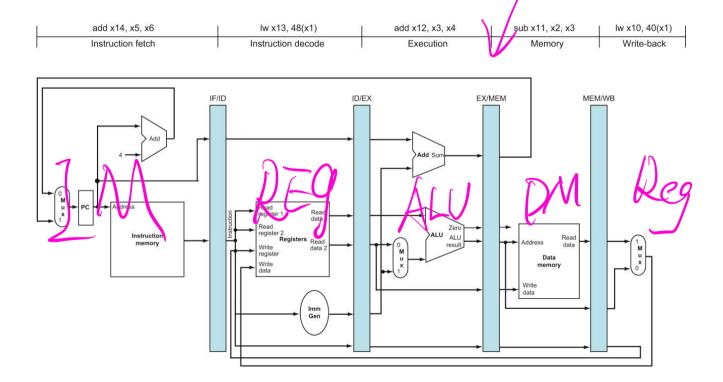
- State of pipeline in a given cycle
 - Instructions flow from left to right
 - Each pipeline stage has all the signals for the instruction in that stage




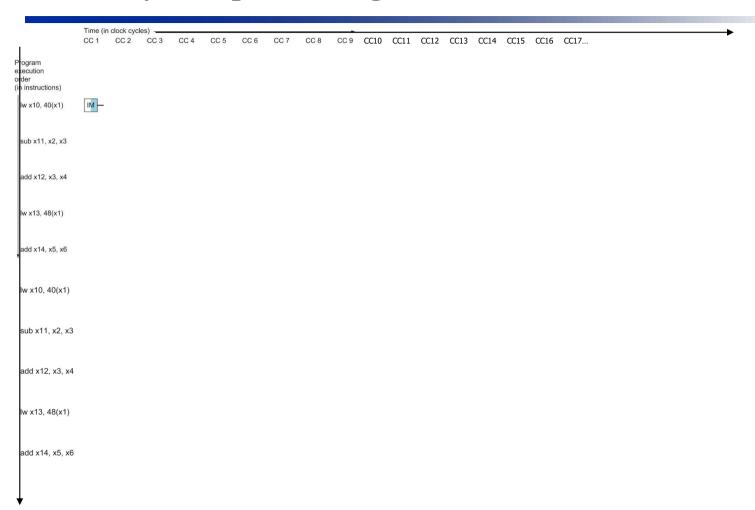


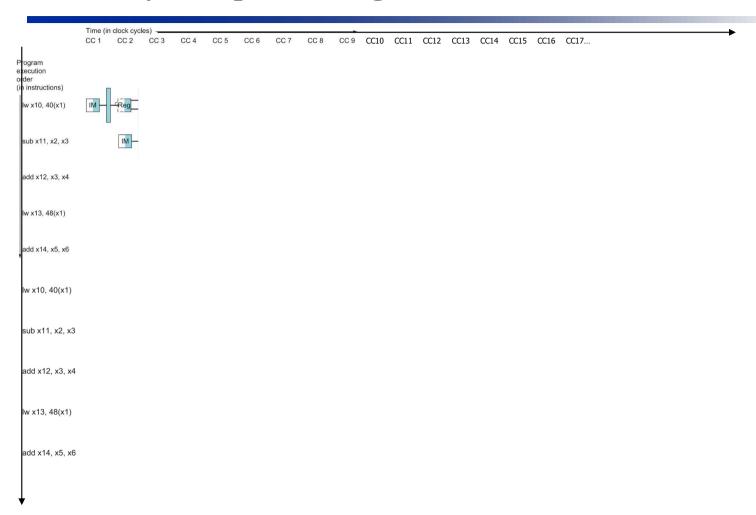


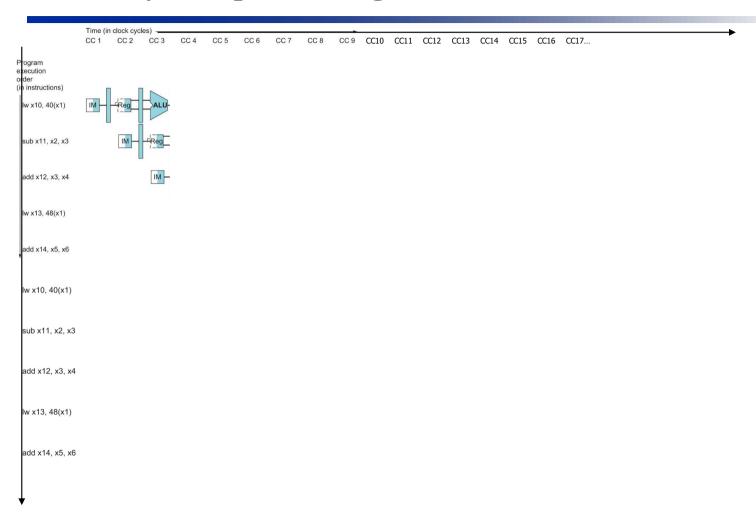


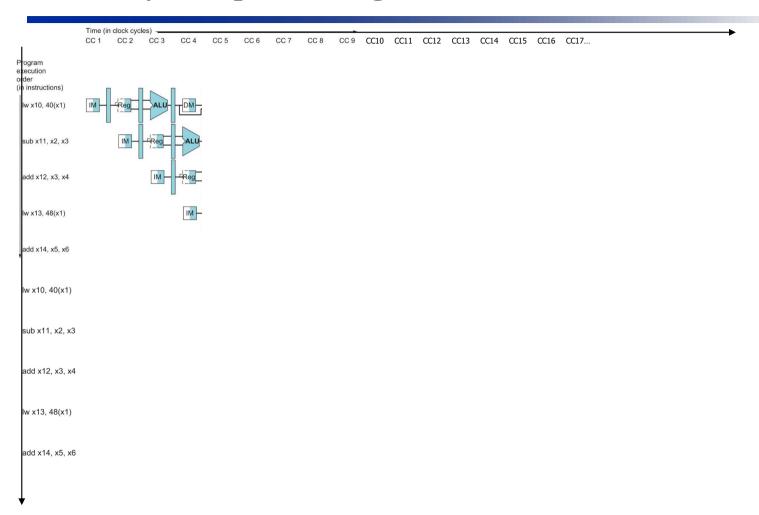


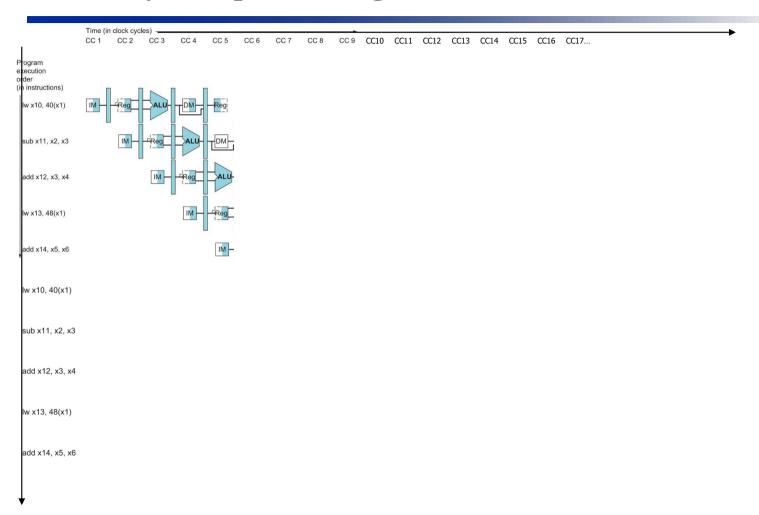


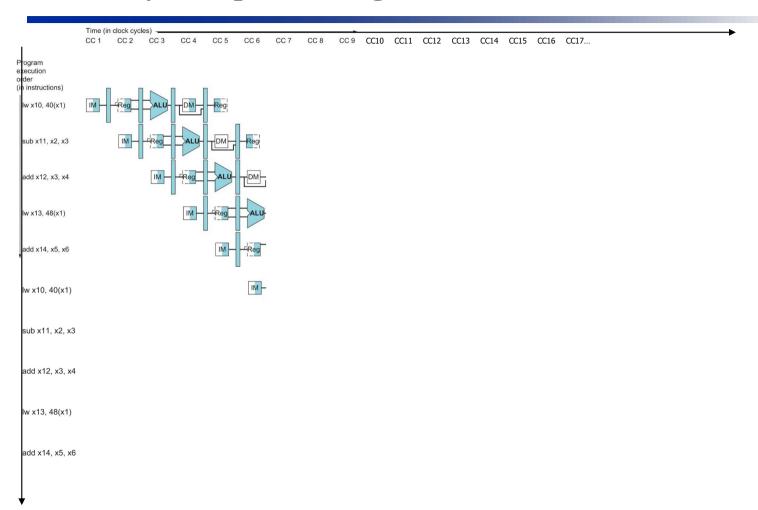


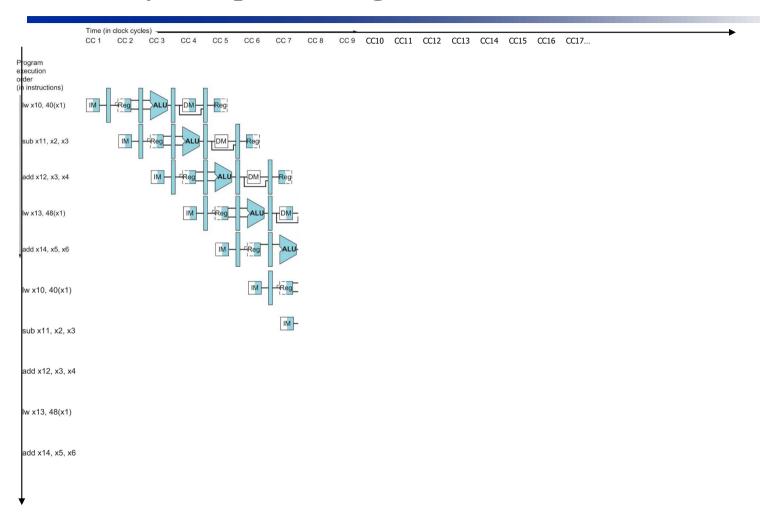


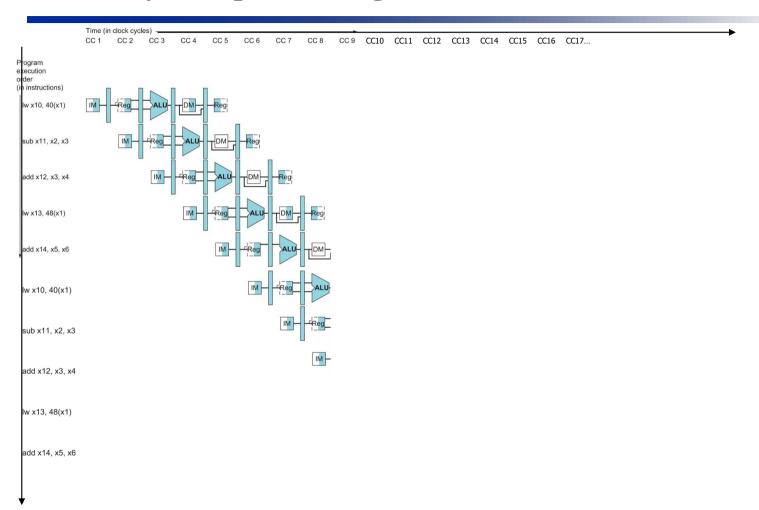


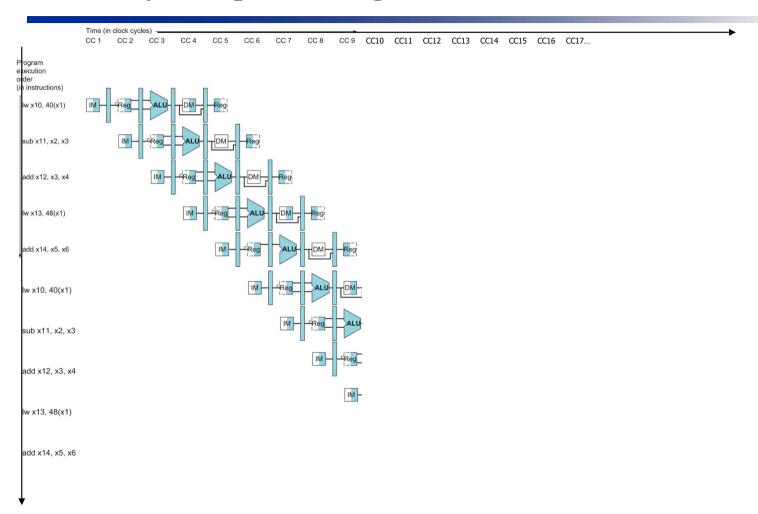


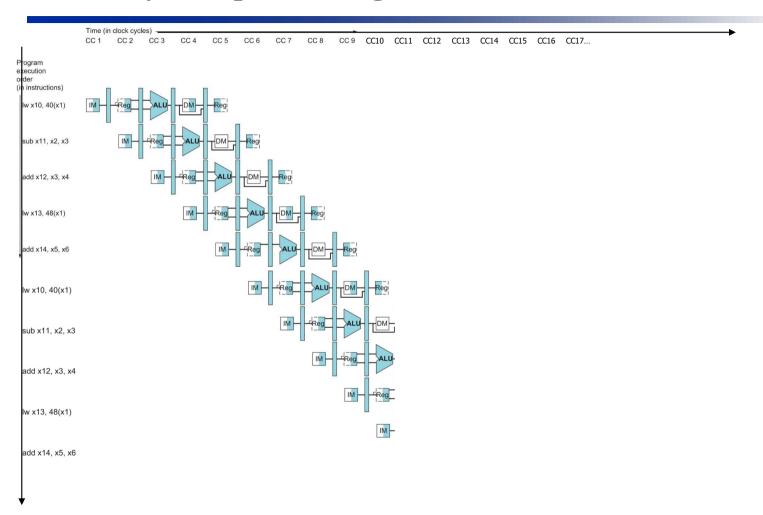


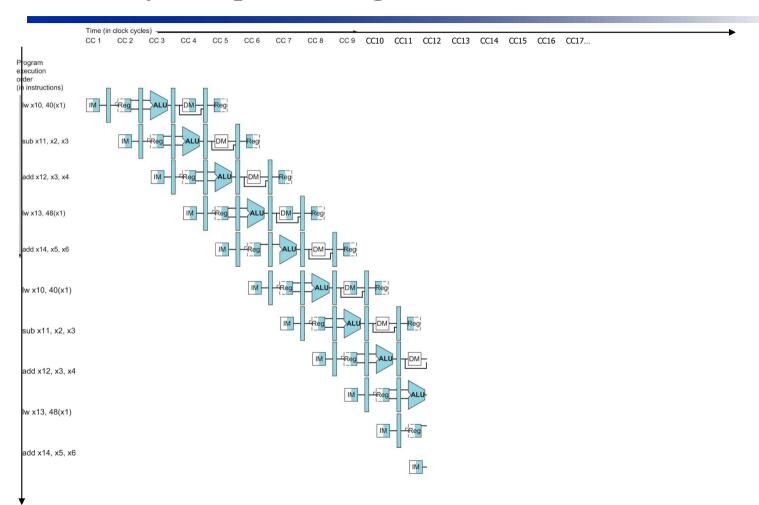


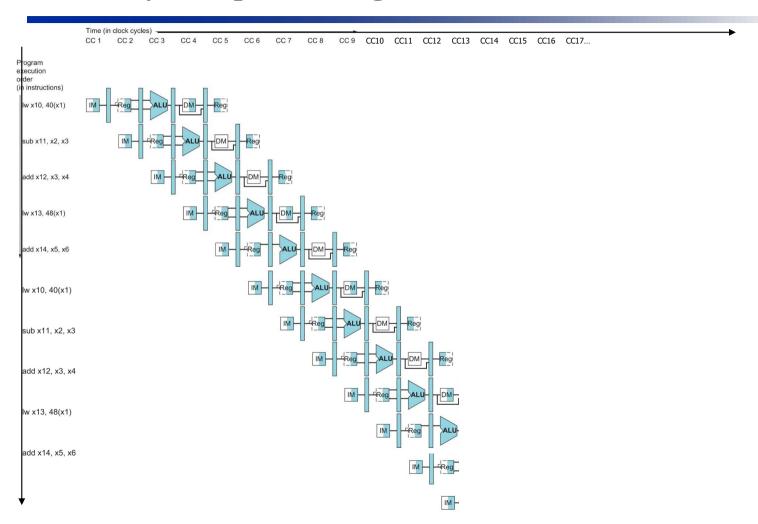


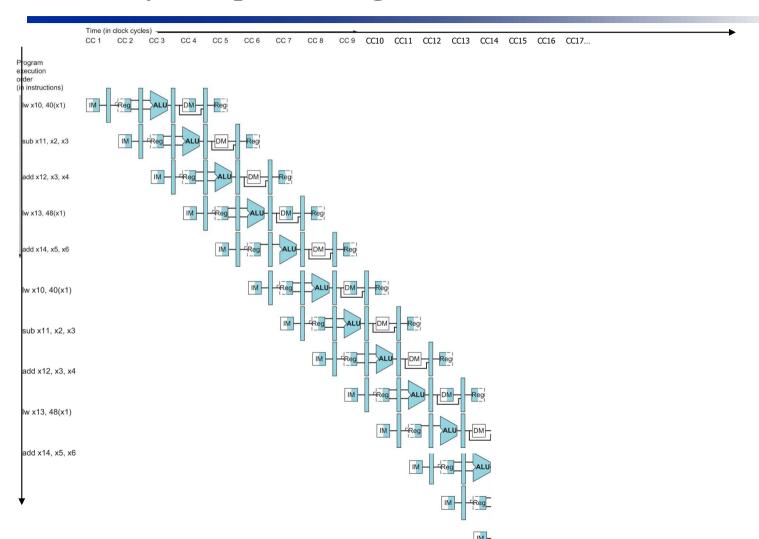

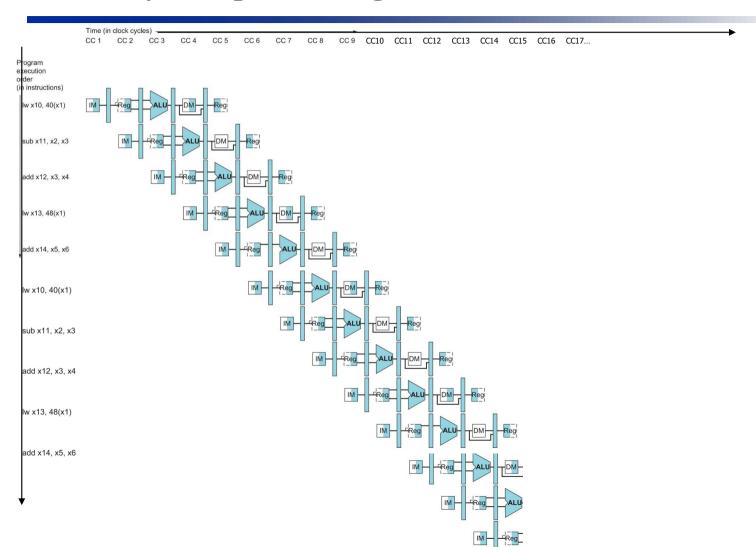

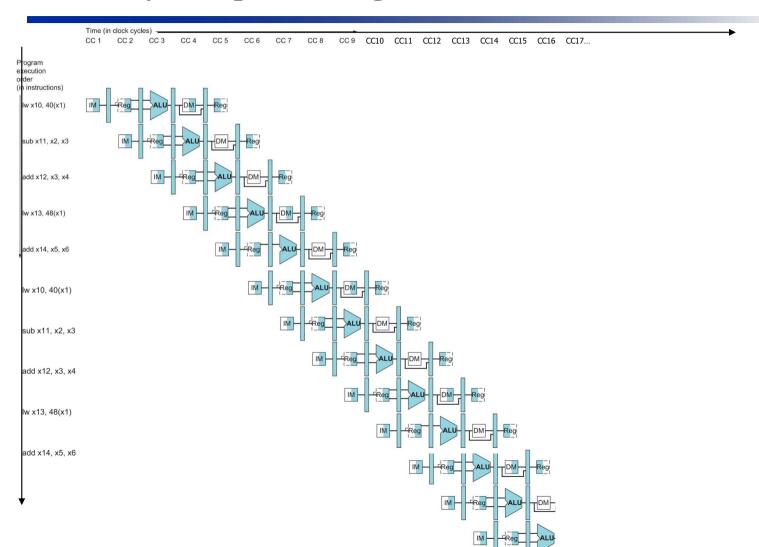


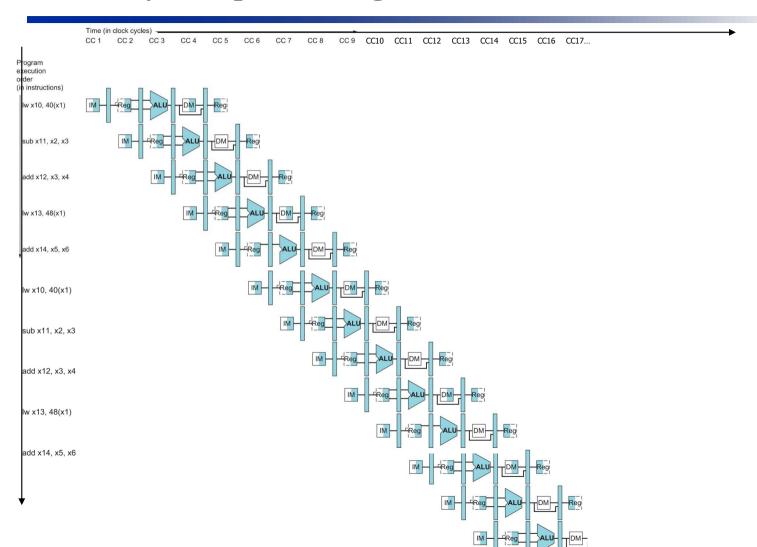

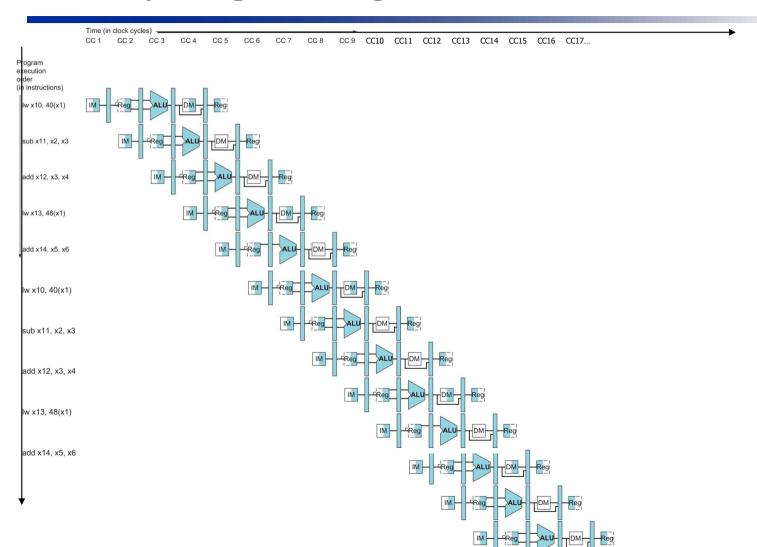

- Showing resource usage in multiple cycles
 - For each instruction, knows when a block is used

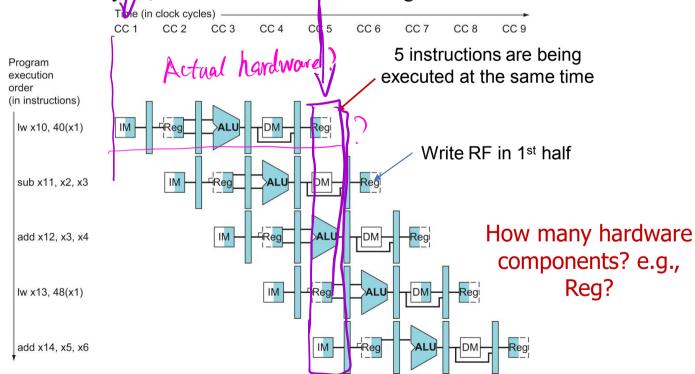For each cycle, knows which block is doing what



Examples of Pipeline Diagram

- Use IF, ID, EX, MEM, WB to indicate pipe stages
 - Sometimes use EXE for EX and ME for MEM

XXXXX						5 instructions are being executed				
		1	2	3	4	5	6	7	8	9
lw	x10,40(x1)	IF	ID	EX	MEM	WB				
sub	x11,x2,x3		IF	ID	EX	MEM	WB			
add	x12,x3,x4			IF	ID	EX	MEM	WB		
lw	x13,48(x1)				IF	ID	EX	MEM	WB	
add	x14,x5,x6					IF	ID	EX	MEM	WB

One of the online chapters shows more detailed pipeline diagrams.

Ch04 e2.pdf (elsevier.com)

Troubles from Pipelining

- Pipeline Hazards
 - Structural hazards: attempt to use the same resource by two different instructions at the same time
 - Data hazards: attempt to use data before it is ready

• An instruction's source operand(s) are produced by a prior instruction still in the pipeline


Control hazards: attempt to make a decision about program control flow before the condition has been evaluated and the new PC target address calculated

• branch and jump instructions, exceptions

Pipeline control must detect and take action to resolve hazards

Potential hazards in pipelined laundry example

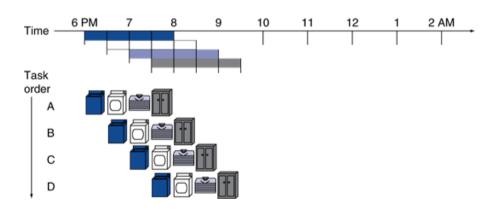
- What if you have a washer and dryer combo?
- What if you are the only person doing the laundry?



Dealing with Hazards


- We can usually resolve hazards by waiting
- We will find better ways to deal with hazards
- Dealing with structural hazards
 - Add more resources
 - Or share resources

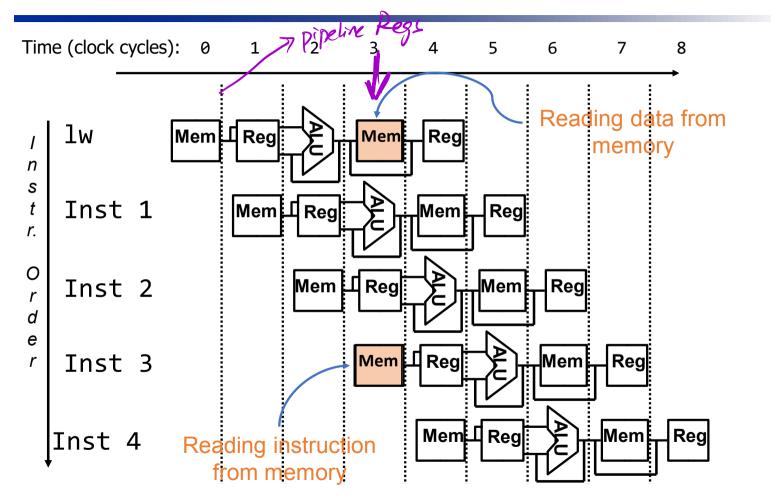A Single Memory Would Be a Structural Hazard



Fix: separate instr and data memories (I\$ and D\$)

How About Register File Access?

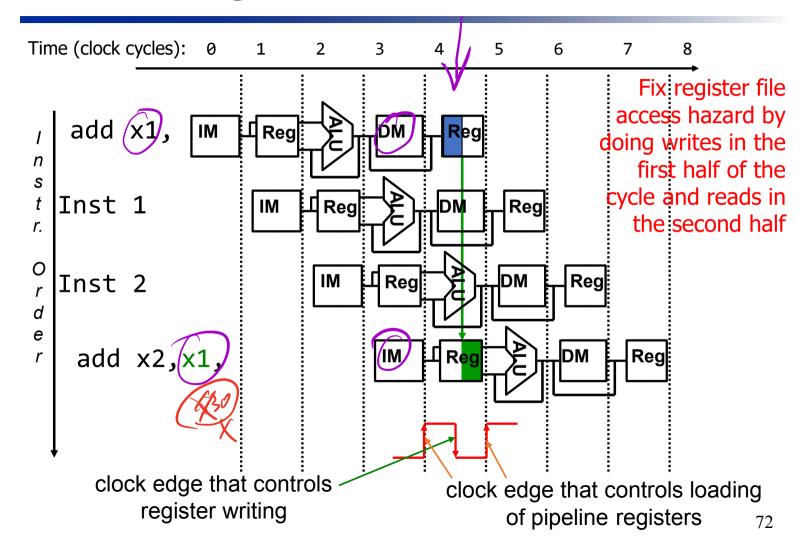

Structural hazards in 5-stage pipeline

- Dealing with structural hazards
 - Add more resources (]M, DM)
 - Or Share resources
- Memory
 - Add more resources: instruction memory and data memory
- Register
 - Share resources: write in the first half of a cycle and read in the second

Pipelining and ISA Design

- RISC-V ISA designed for pipelining
 - All instructions are 32-bits
 - Easier to fetch and decode in one cycle
 - c.f. x86: 1- to 17+ bytes instructions
 - Few and regular instruction formats
 - Can decode and read registers at the same time
 - Load/store addressing
 - Can calculate address in 3rd stage, access memory in 4th stage

Question

- In which stage are the control signals generated?
- A. IF
- B. ID
- C. EX
- D. MEM
- E. It depends on instruction types

Question

- In which stage is RegWrite used?
- A. IF
- B. ID
- C. EX
- D. MEM
- E. WB

Timing of writing to register file

